

EECS251B : Advanced Digital Circuits and Systems

Lecture 15 – Latches

Borivoje Nikolić



The Startup Flipping Nvidia's Playbook on its Head

March 5, 2024, The Information. Taalas is developing the exact opposite of customizable chips: rigid chips which are each specialized for a different AI model, whether it's Meta Platforms' Llama models or Stable Diffusion. The Toronto-based startup, which was founded in August last year by former Nvidia and AMD veteran Ljubisa Bajic, raised \$12 million in September and \$38 million in February from Quiet Capital and Pierre Lamond, an advisor at Eclipse Ventures who was previously a general partner at Khosla Ventures and Sequoia Capital.



Taalas cofounder and CEO Ljubisa Bajic. Courtesy of Taalas.



Announcements

- Lab 5 still waiting on PDK correction
 - The newest fix brings it very close
- Start project phase 1
 - Spec doc due tomorrow
- Homework 2 due tomorrow
 - Quiz 2 on March 12
 - Homework 3 posted this week





Latch Timing

Latch Sequencing

  


Latch-Based Timing

- Single-phase, two-latch

  

As long as transitions are within the assertion period of the latch, no impact of position of clock edges

Latch Design and Hold Times

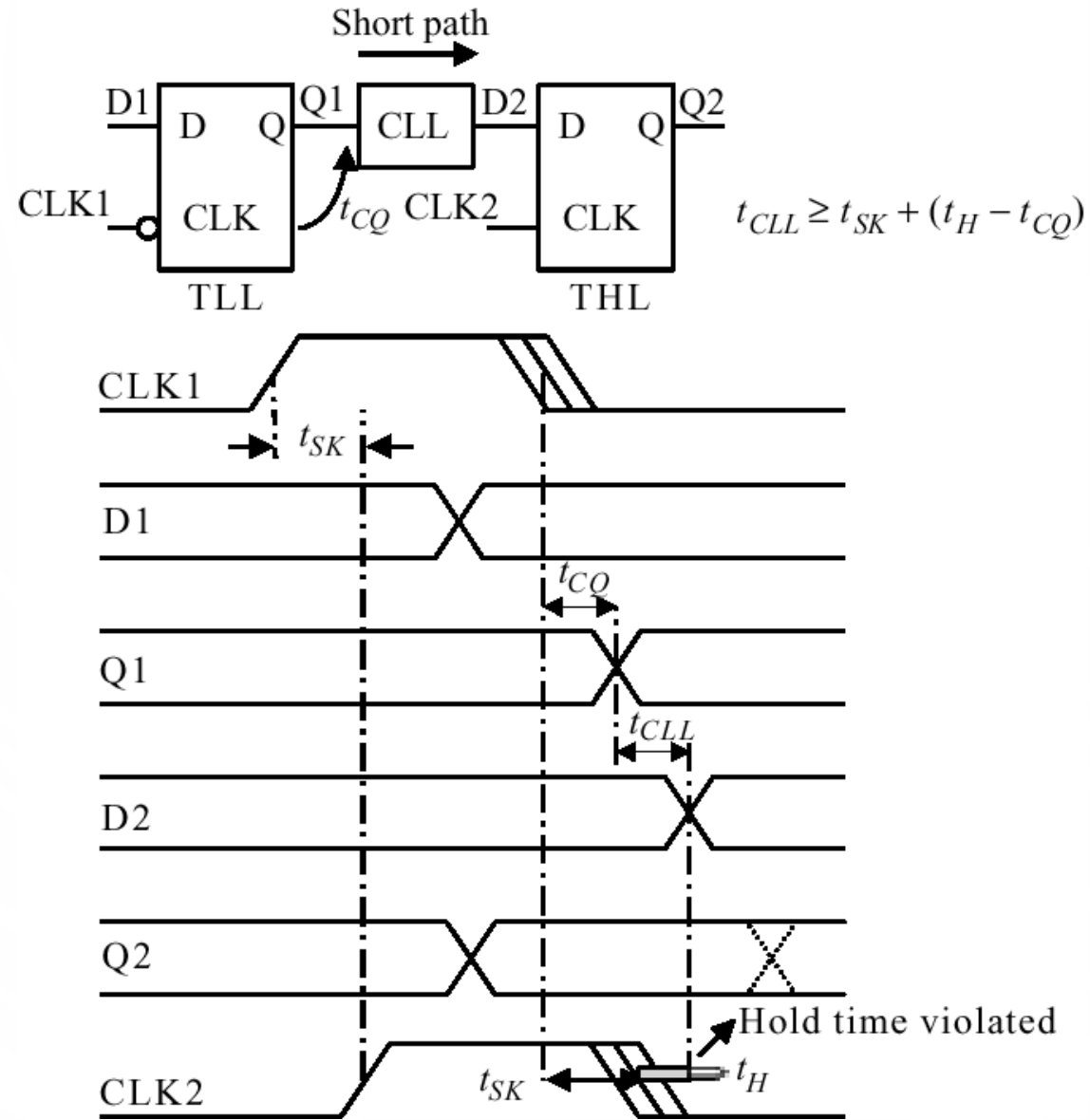


Soft-Edge Properties of Latches


- **Slack passing** – logical partition uses left over time (slack) from the *previous* partition
- **Time borrowing** – logical partition utilizes a portion of time allotted to the *next* partition
- Makes most impact in unbalanced pipelines

Bernstein et al, Chapter 8, Chandrakasan, Chap 11 (by Partovi)

Slack Passing and Time Borrowing

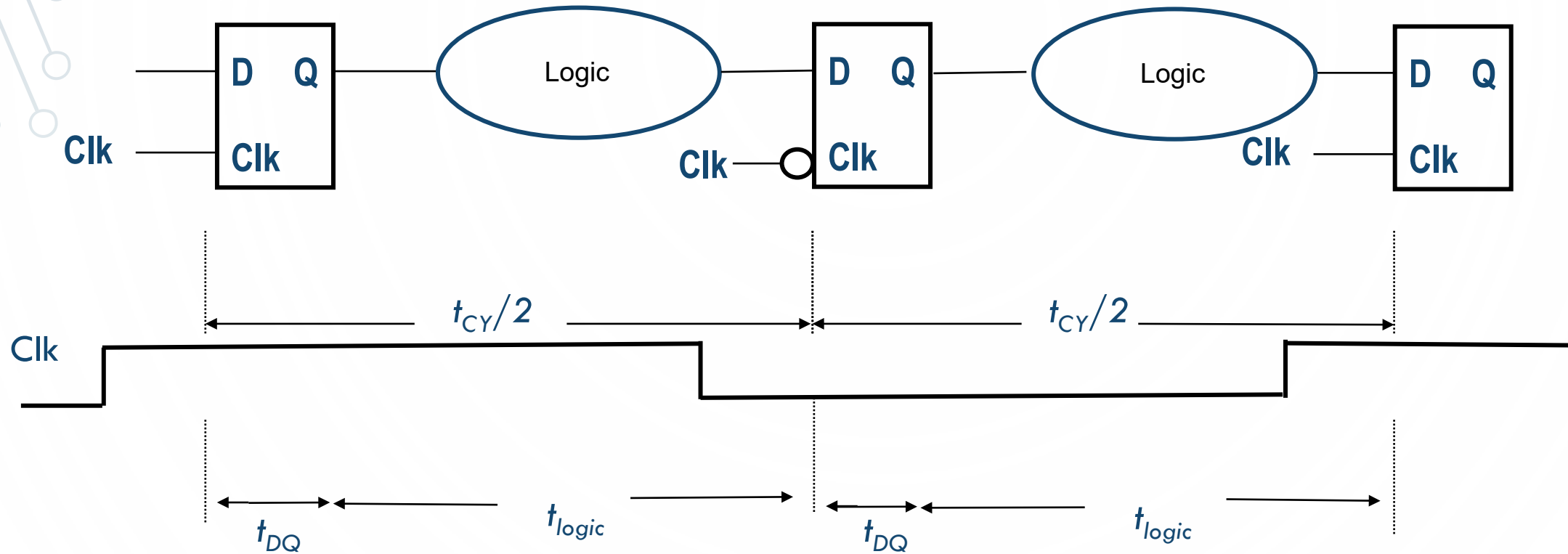


Slack Passing and Time Borrowing

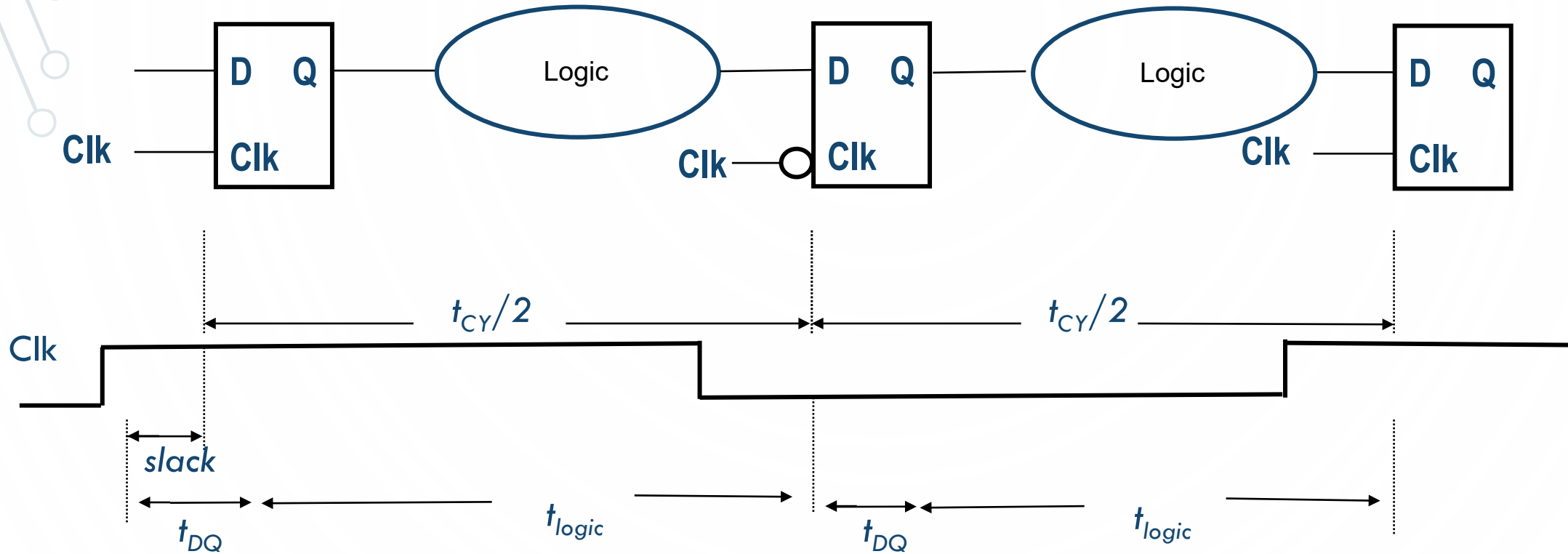


- Slack passed

Slack Passing and Time Borrowing

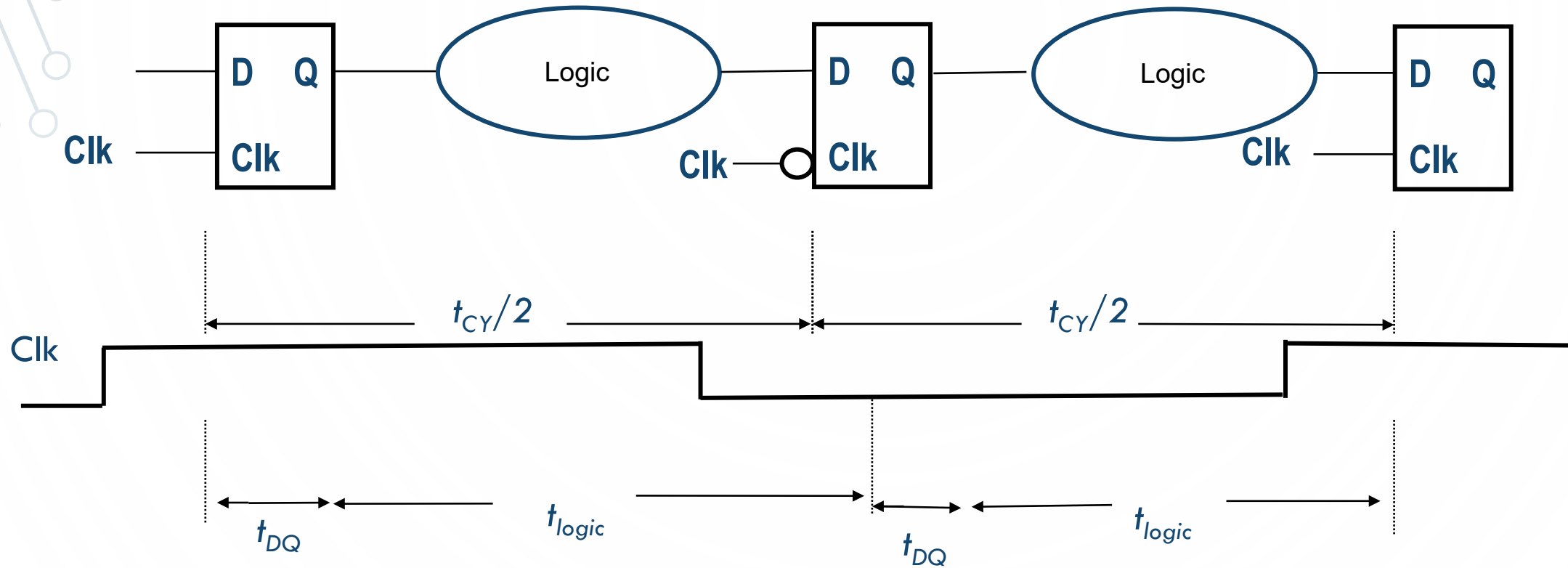

- Time borrowed

Slack-Passing and Cycle Borrowing

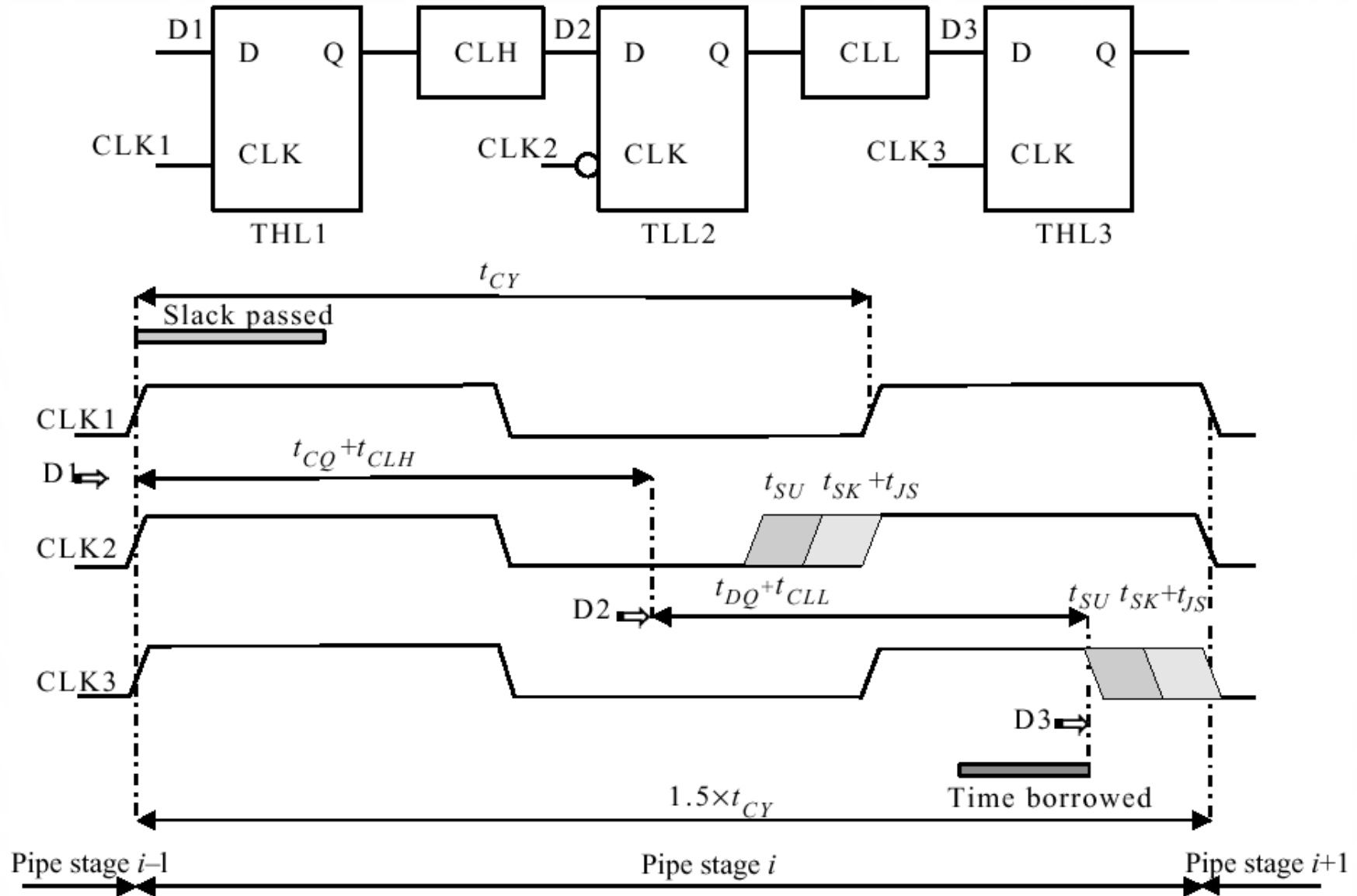

For N stage pipeline, overall logic delay should be $< N T_{cl}$






Design for Performance

Latch Design



Review: MUX

- 2-input MUX

   


Review: MUX

- 2-input MUX





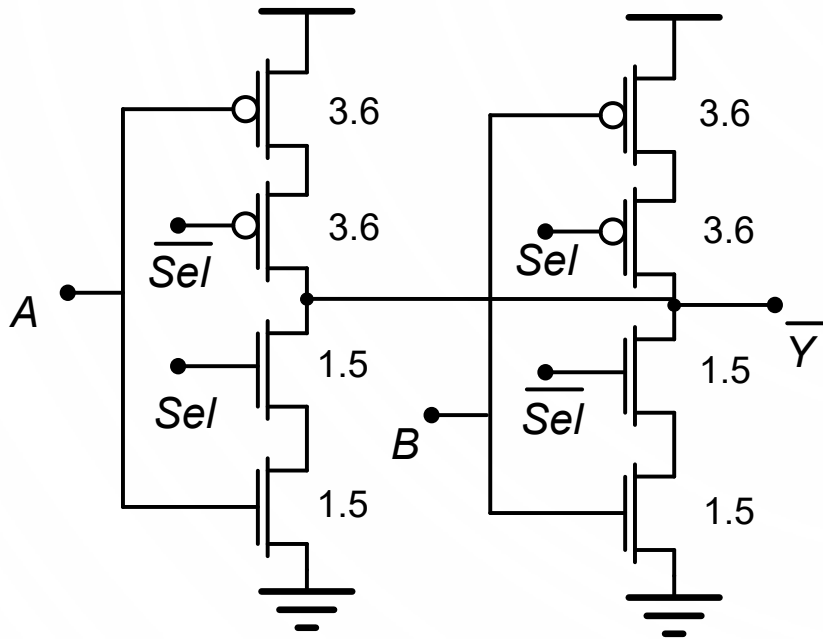
 


$$g_A = 1.7$$
$$g_B = 1.7$$
$$g_{Sel} = 3.4$$





$$p_{C2MOS} = 1.7$$
$$p_{MUX} = 3.4$$

 


Review: Transmission Gates

      

Review: Transmission Gates

    




Review: Transmission Gates

 

$$g_A \sim 1.7$$


$$g_S = 1.7$$

   $p = 1.7$ (but larger in practice because of layout)



Generating Complementary Clocks


- Inverter fork

 

$$g_{\text{fork}} \sim 1$$

$$p_{\text{fork}} \sim 3$$


Latch vs. Flip-Flop

 

Courtesy of IEEE Press, New York. © 2000


Latches

Transmission-Gate Latch

 


Usually without contention


C²MOS Latch

 


Latches

 

(a) The transparent high latch (THL)

 

(b) The transparent low latch (TLL)

 

(c) Timing waveforms for the THL




Design for Performance

Delay, Setup, Hold


Setup-Hold Time Illustrations

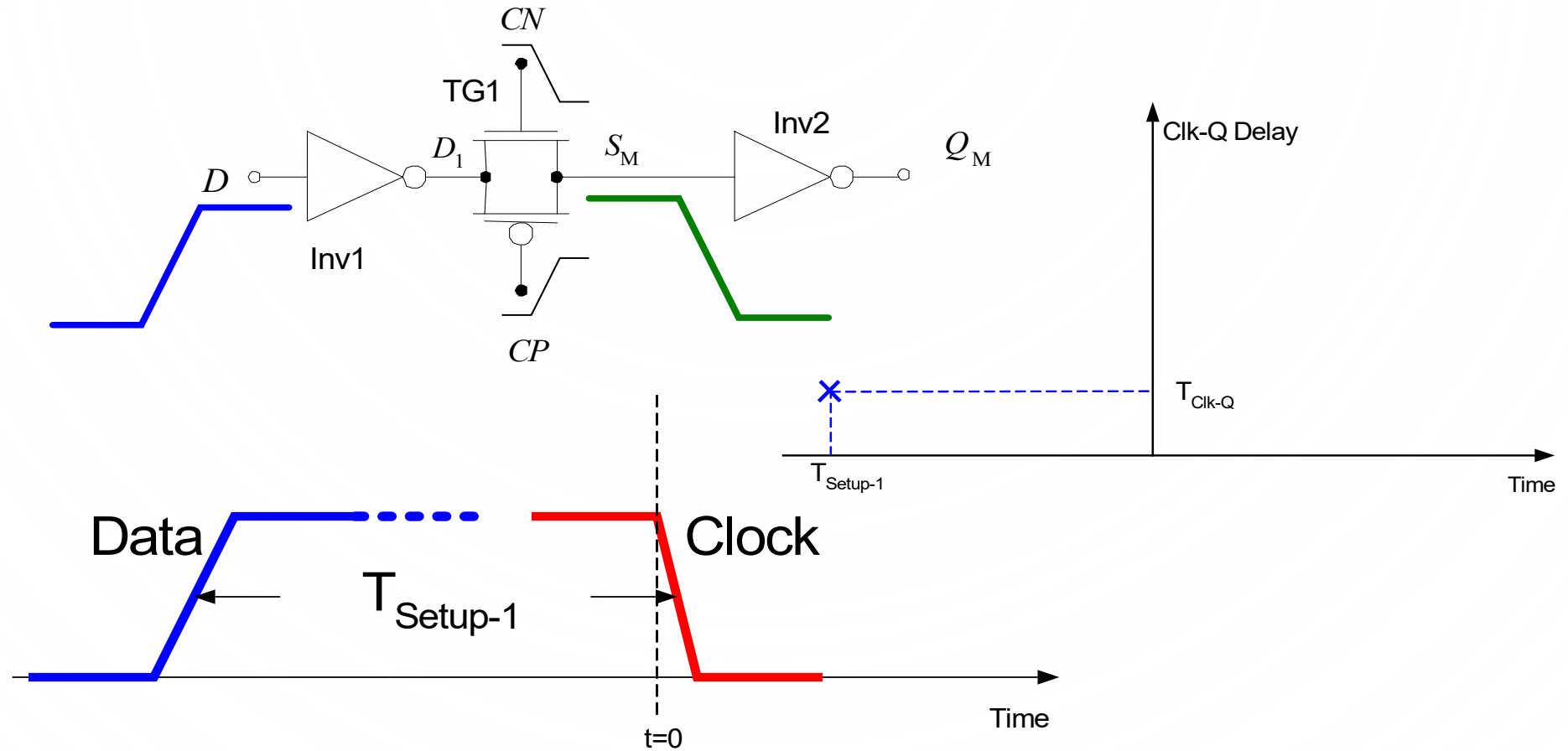Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

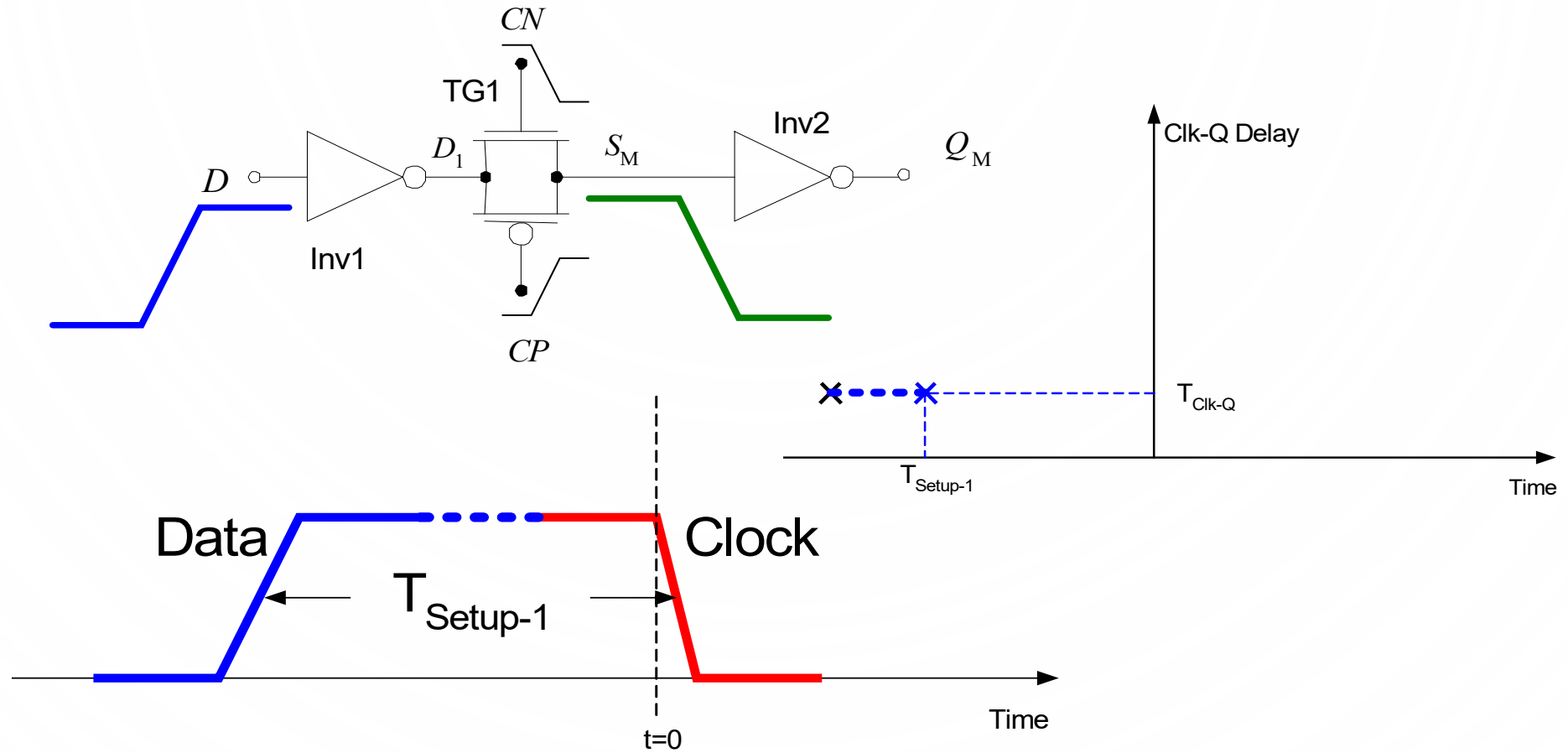Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

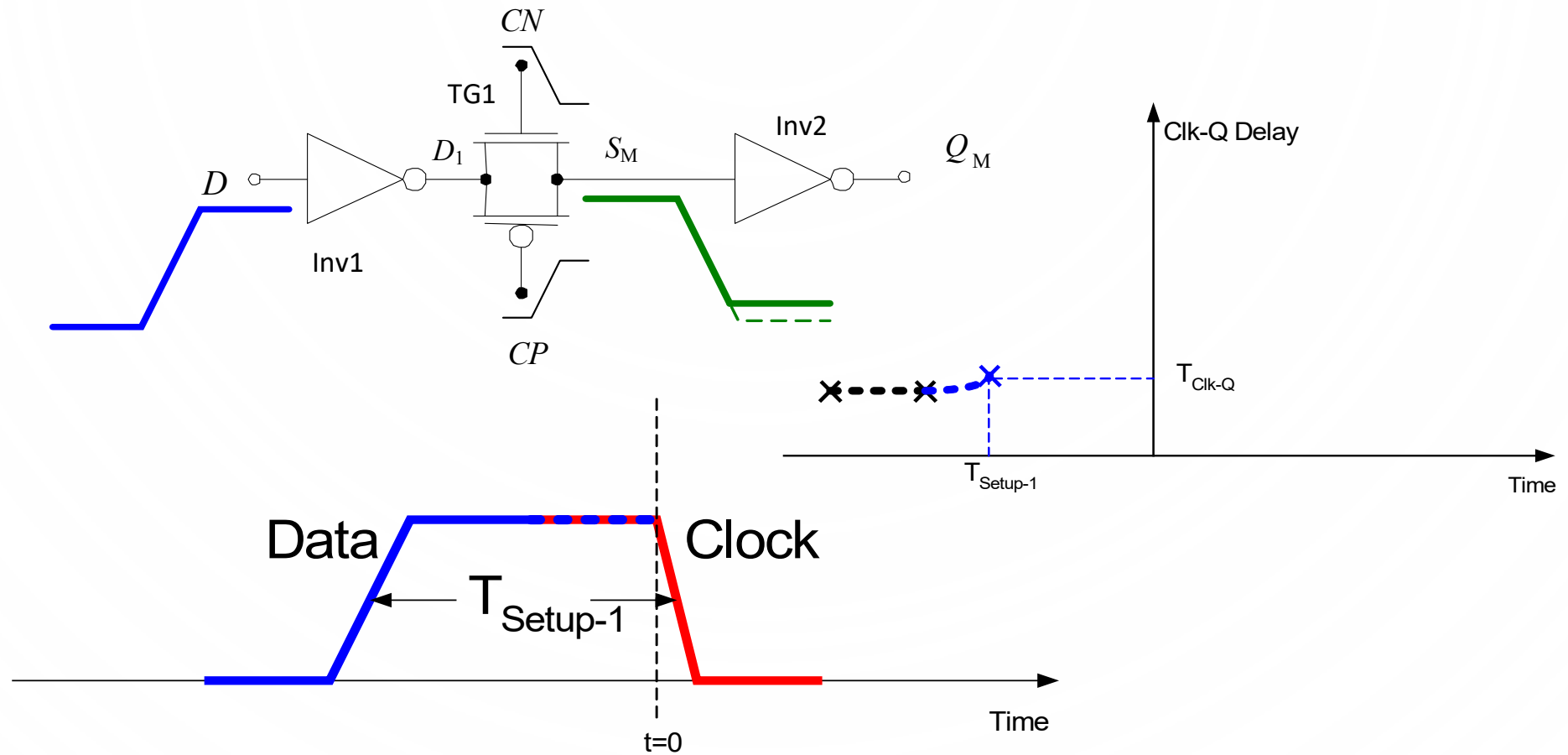Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

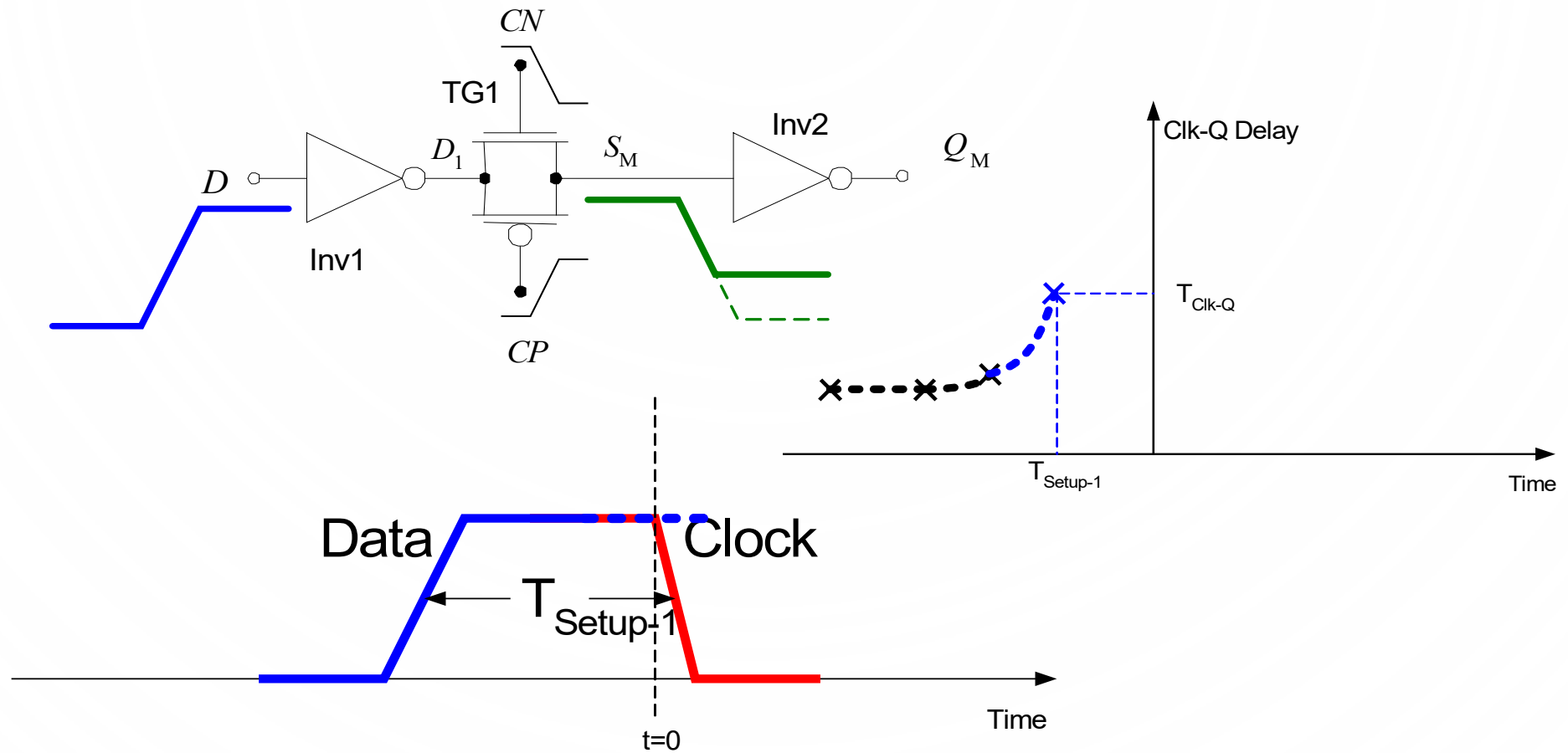Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

 Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

Hold-1 case

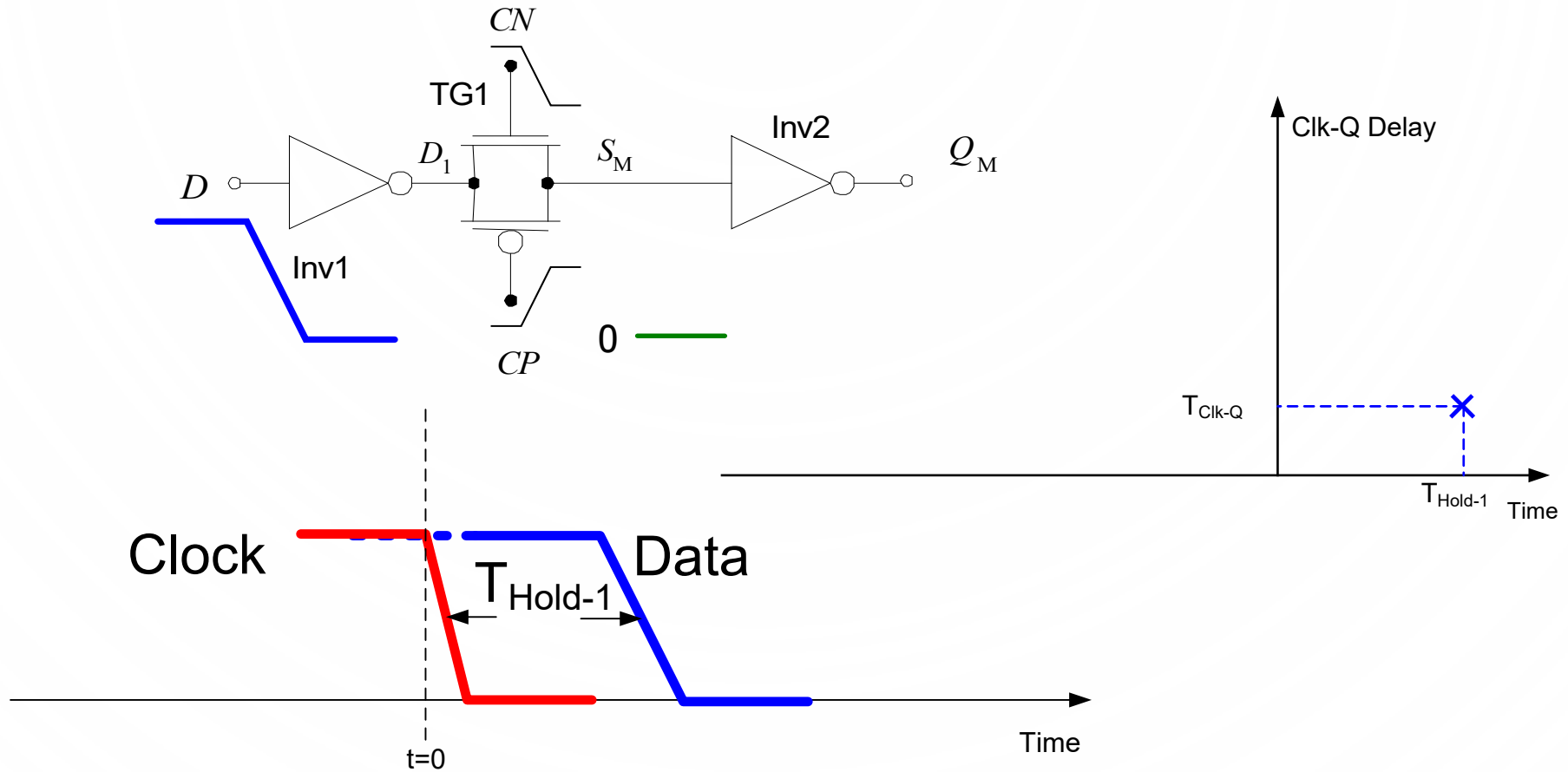




Setup-Hold Time Illustrations

Hold-1 case

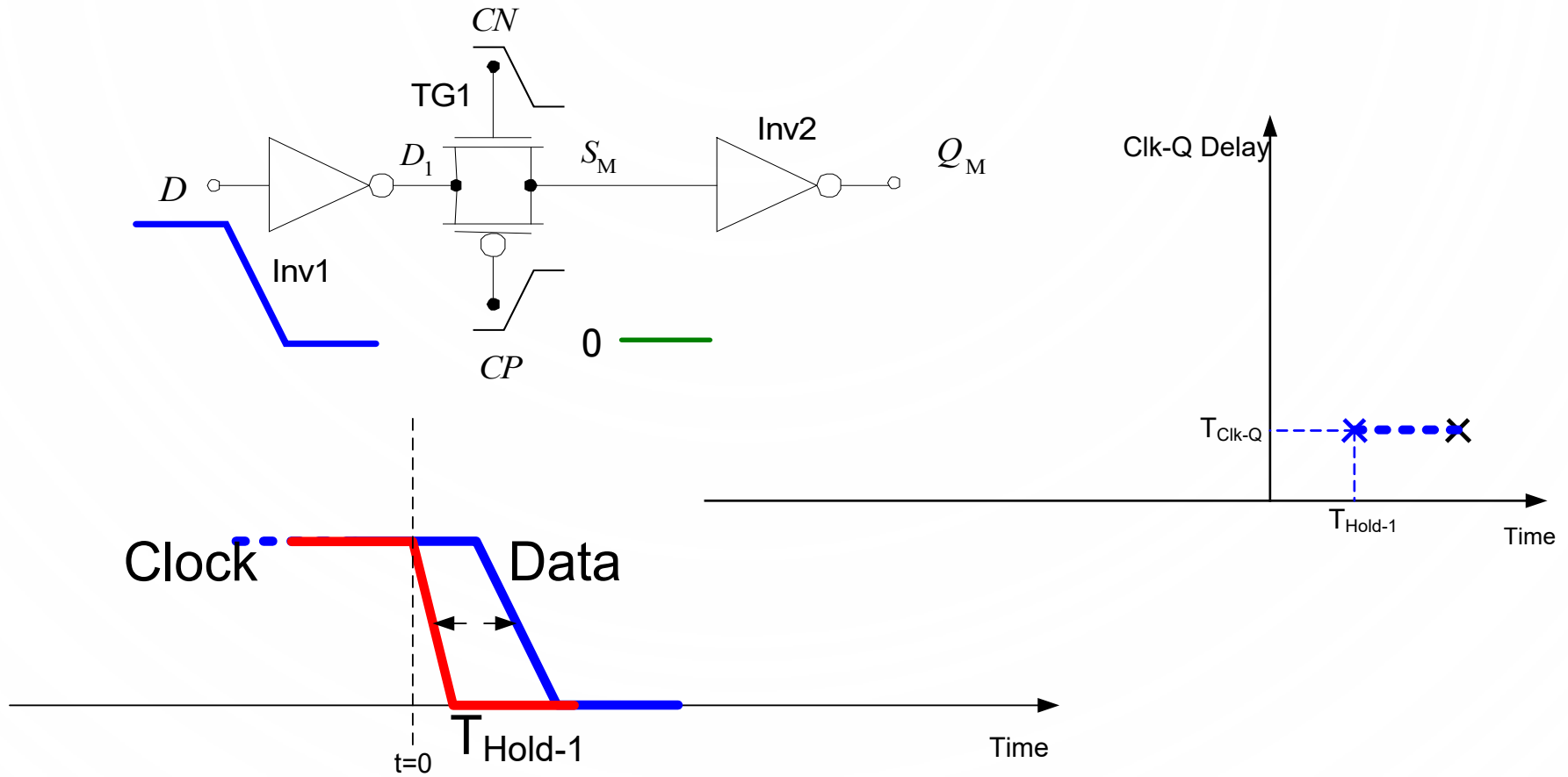


Setup-Hold Time Illustrations

Hold-1 case

  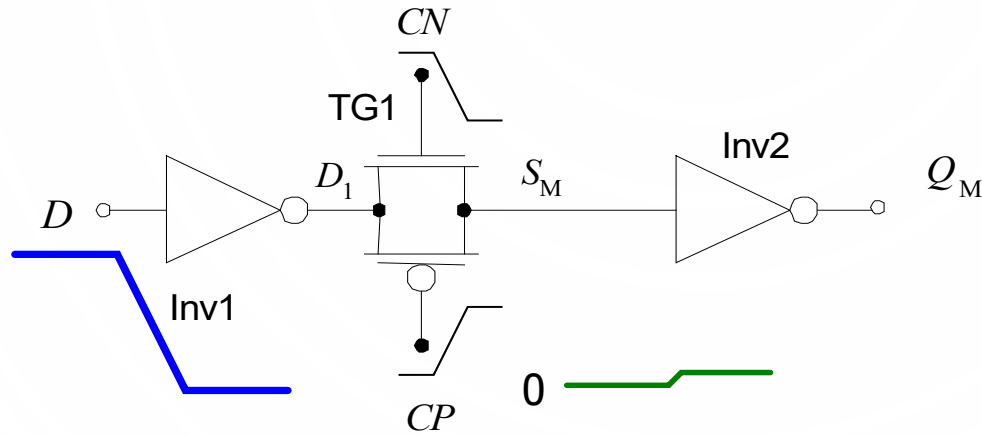


Setup-Hold Time Illustrations

Hold-1 case


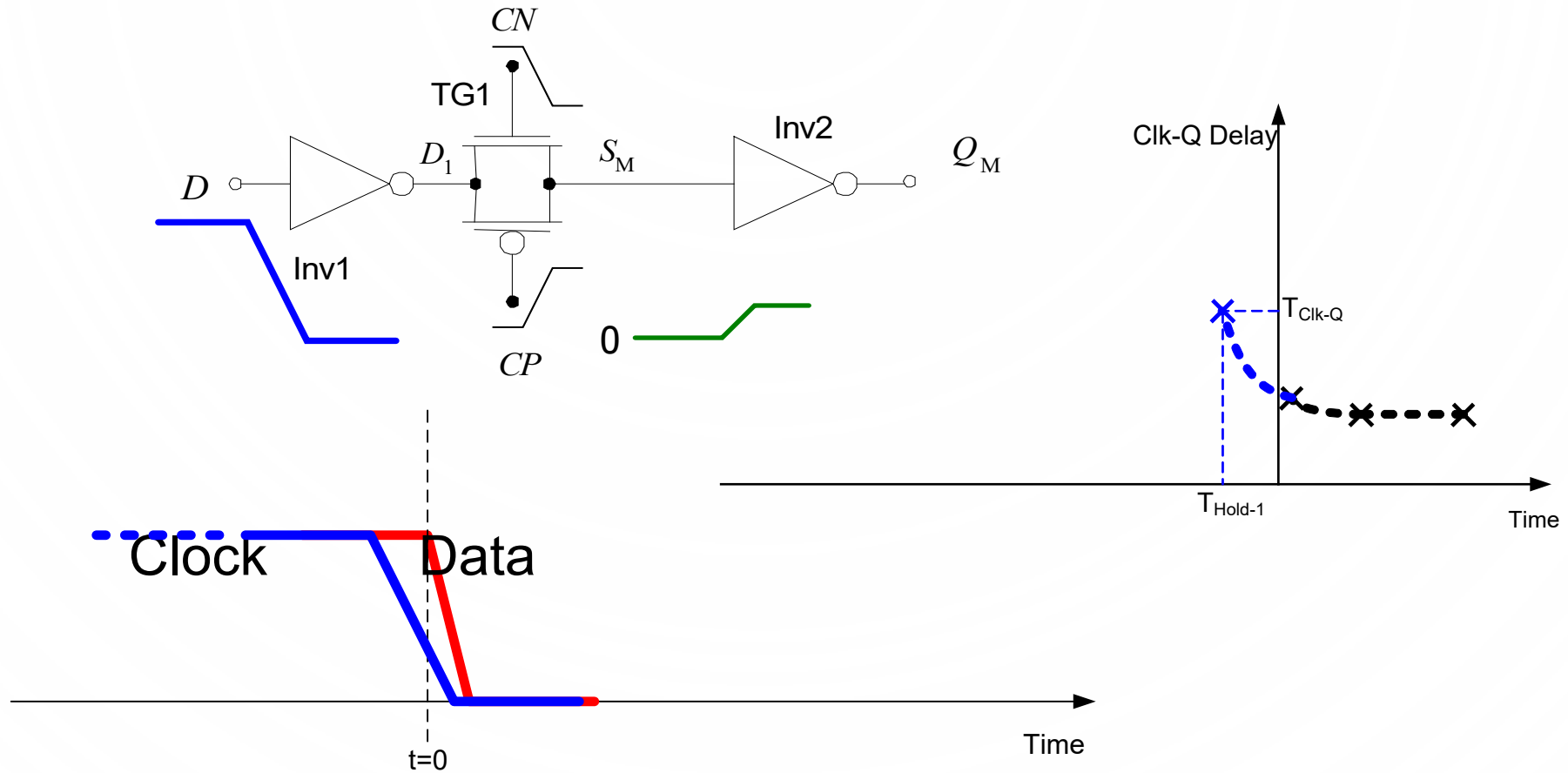


Setup-Hold Time Illustrations


Hold-1 case

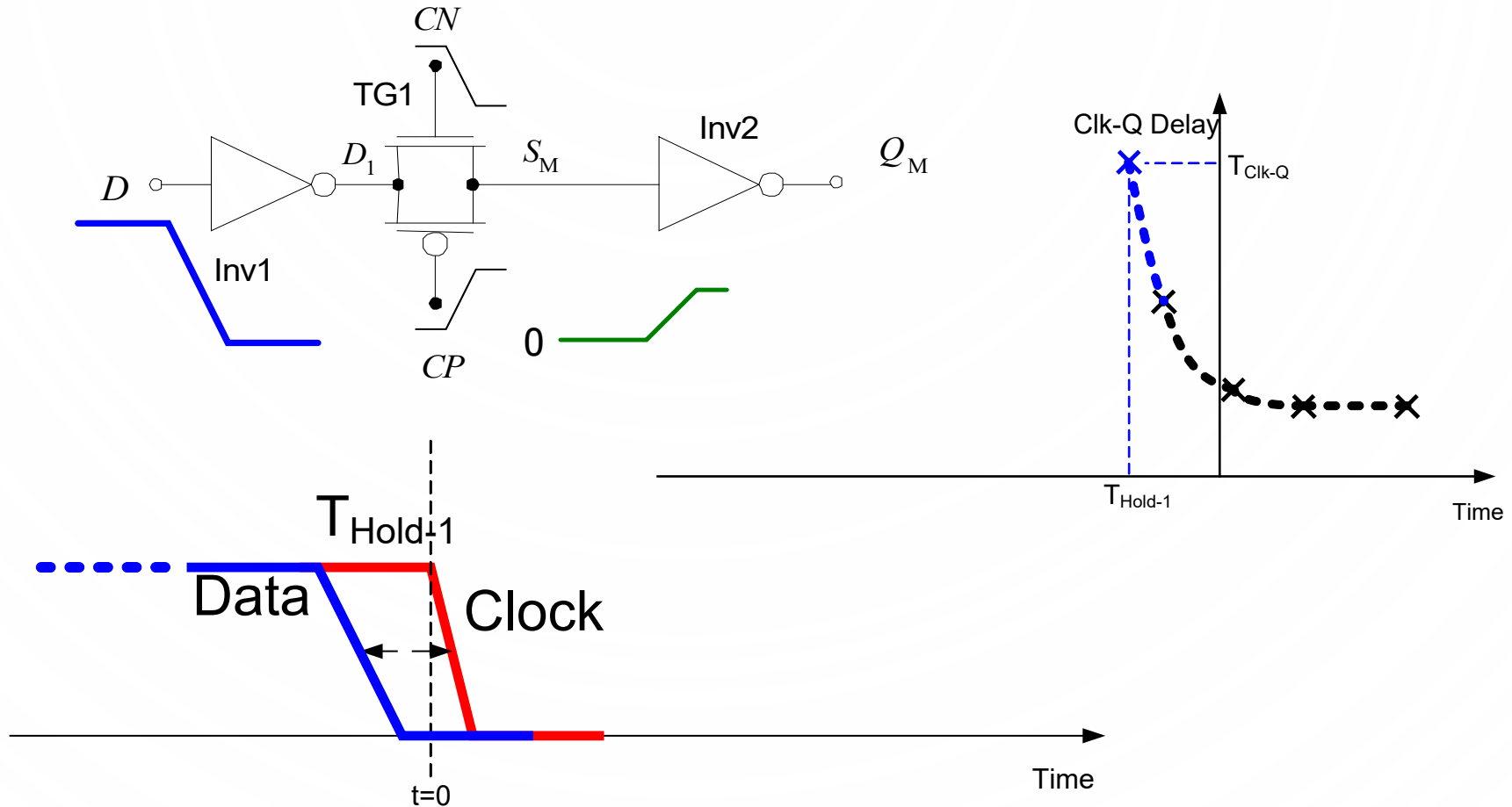

More Precise Setup Time

  

Latch t_{D-Q} and t_{Clk-Q}

 


(ignore feedback inverters, assume $g_{fork}=1$)

$$t_{Clk-Q} = g_1 f_1 + p_1 + g_2 f_2 + p_2; \quad g_1 f_1 = g_2 f_2 = \sqrt{GF}$$

Assume $F = 1$, for simplicity, (although a latch should drive $F > 4$)

$$\sqrt{GF} = 1.3$$
 
$$t_{Clk-Q} = (1.3 + 1.7) + (1.3 + 1) = 5.3 (=1.06 \text{ FO4})$$





$$g_1 = 1.7 \quad g_2 = 1$$

$$p_1 = 1.7 \quad p_2 = 1$$

(FO4 inverter delay = $1 + 4 = 5$ unit delays)

t_{setup}

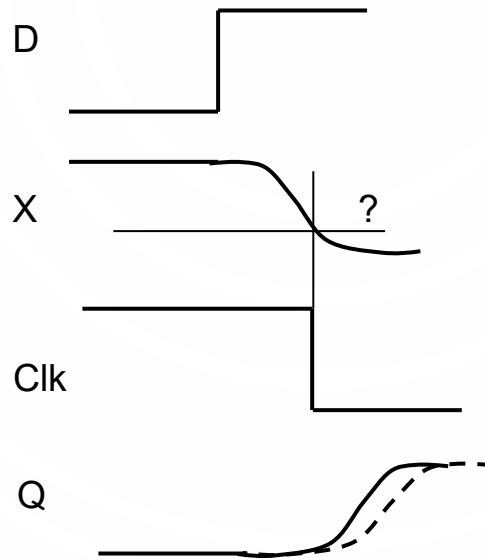 

$3t_u$



$2.3t_u \rightarrow 2.58t_u$ For $1.05 t_{\text{clk-Q}}$

12% delay increase

To find the setup time, we will find the D-Clk offset that increases $t_{\text{clk-Q}}$ by 5%
 Overall delay is $5.8t_u$, 5% increase is $0.28t_u$

Note: Voltage level of $.12V_{\text{DD}}$ at X causes $\sim 12\%$ delay increase

t_{setup}

  

Assuming exponential response

$$T_{\text{setup}} = -\ln(0.12) \tau = 2.1 \tau$$

$$T_{\text{setup}} = 2.1 \tau = 3t_{\text{prop}} \quad (t_{\text{prop}} = 0.7\tau)$$

$$T_{\text{setup}} = 3 \times 3t_u = 9t_u$$

$$T_{\text{setup}} = 1.8 \text{ FO4}$$

$3t_u$ $2.3t_u \rightarrow 2.58t_u$ For $1.05 t_{\text{clk-Q}}$

11% delay increase

Voltage level of $.12V_{\text{DD}}$ at X causes $\sim 12\%$ delay increase

$$T_{\text{setup}} + T_{\text{Clk-Q}} = 2.8 \text{ FO4}$$

$T_{\text{setup}} + T_{\text{Clk-Q}}$ is typically 2.5-3.5 FO4 for fast latches (with low fanout)



Flip-Flops


Flip-Flops

- Performance metrics
- Delay metrics
 - Insertion delay
 - Inherent race immunity
 - ‘Softness’ (Clock skew absorption)
 - Inclusion of logic
 - Small (+constant) clock load
- Power/Energy Metrics
 - Power/energy
- Design robustness
 - Noise immunity


Types of Flip-Flops

- Two ways to design a flip-flop
 - Latch pair (large majority)
 - Pulsed latch

Latch Pair

 


Pulse-Triggered Latch

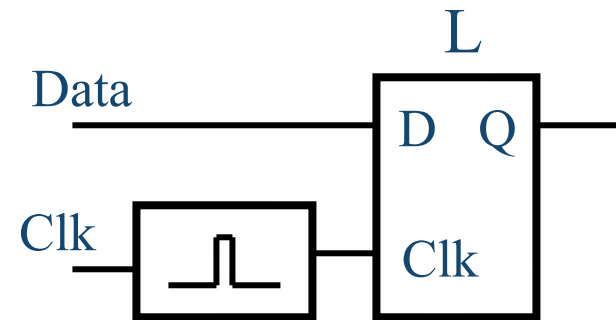

Flip-Flop (Latch Pair) Clk-Q, setup, hold

 Calculation is nearly identical to that of a latch (ignore feedback inverters).
 t_{Clk-Q} is the delay of the second latch, which is about 1FO4;
 note that t_{Ck-Q} should include the delay of the inverter fork



Setup time calculation goes the same way!

$t_{setup} : t_D - t_{Ck}$
 Difference to cause T_{Ck-Q} increase by 5% by affecting the storage node

Flip-Flop Library Timing Characterization



- Combinational logic delay is a function of output load and input slope
- Sequential timing (flip-flop):
 - $t_{\text{clk-q}}$ is function of output load and clock rise time
 - $t_{\text{Su}}, t_{\text{H}}$ are functions of D and Clk rise/fall times
 - Flip-flop has multiple stages, so the delay is less sensitive to input slope

Pulse-Triggered Latches

- First stage is a pulse generator
 - generates a pulse (glitch) on a rising edge of the clock
- Second stage is a latch
 - captures the pulse generated in the first stage
- Pulse generation results in a negative setup time
- Frequently exhibit a soft edge property
- Note: power is always consumed in the pulse generator
 - Often shared by a group (register)


Pulsed Latch

Simple pulsed latch

 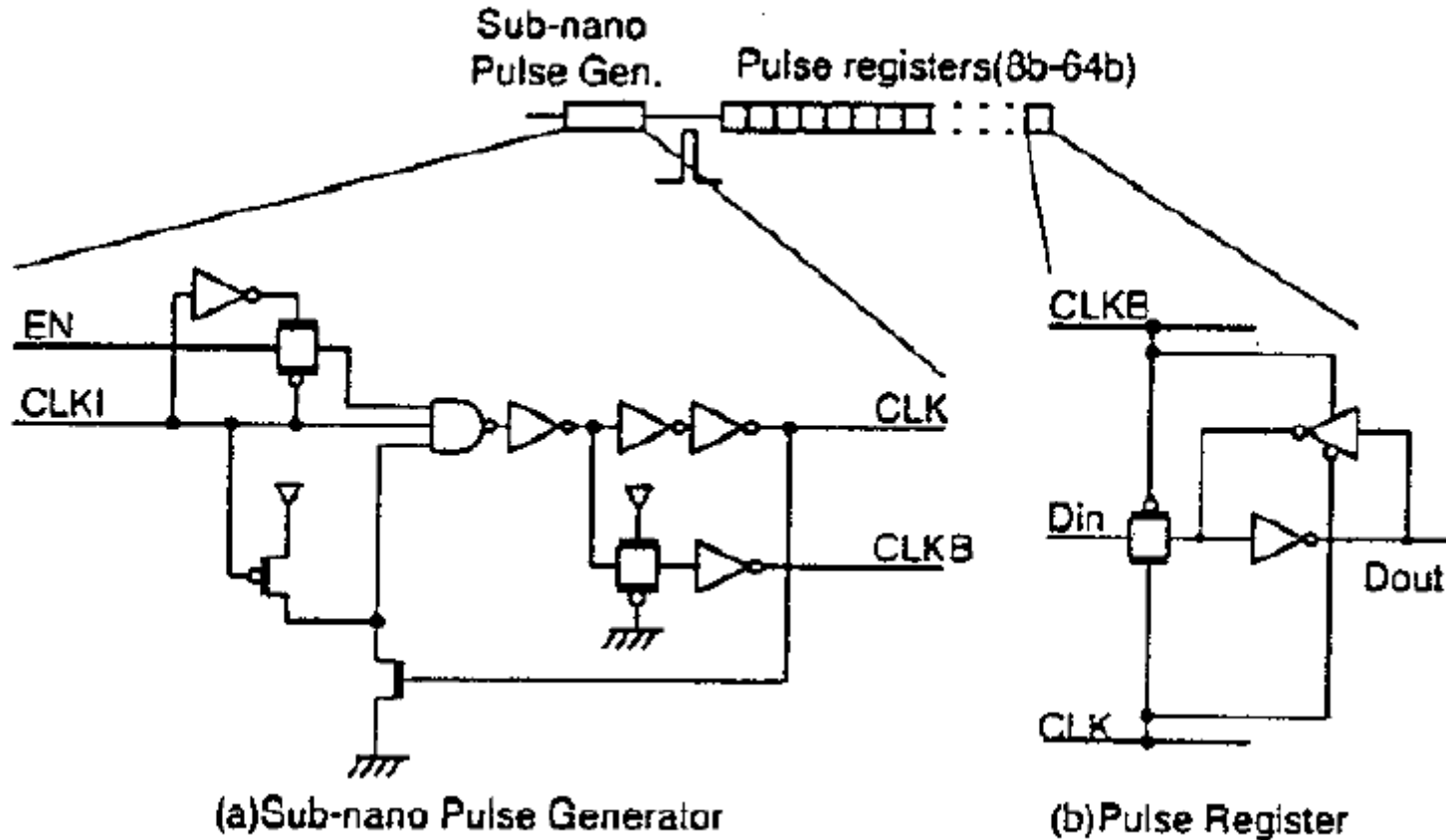

Kozu, ISSCC'96


Intel/HP Itanium 2

 

Naffziger, ISSCC'02


Pulsed Latches

 Hybrid Latch Flip-Flop, AMD K-6
Partovi, ISSCC'96



HLFF Operation

 1-0 and 0-1 transitions at the input with 0ps setup time




VDD=2.3v, 85°C, Typical Devices
C_{clk} = 60ff, C_{qb} = 300ff

T_{cq} = T_{dq} = 340ps
T_{hold} = 180ps
T_{su(min)} = -90ps

Hybrid Latch Flip-Flop


Skew absorption

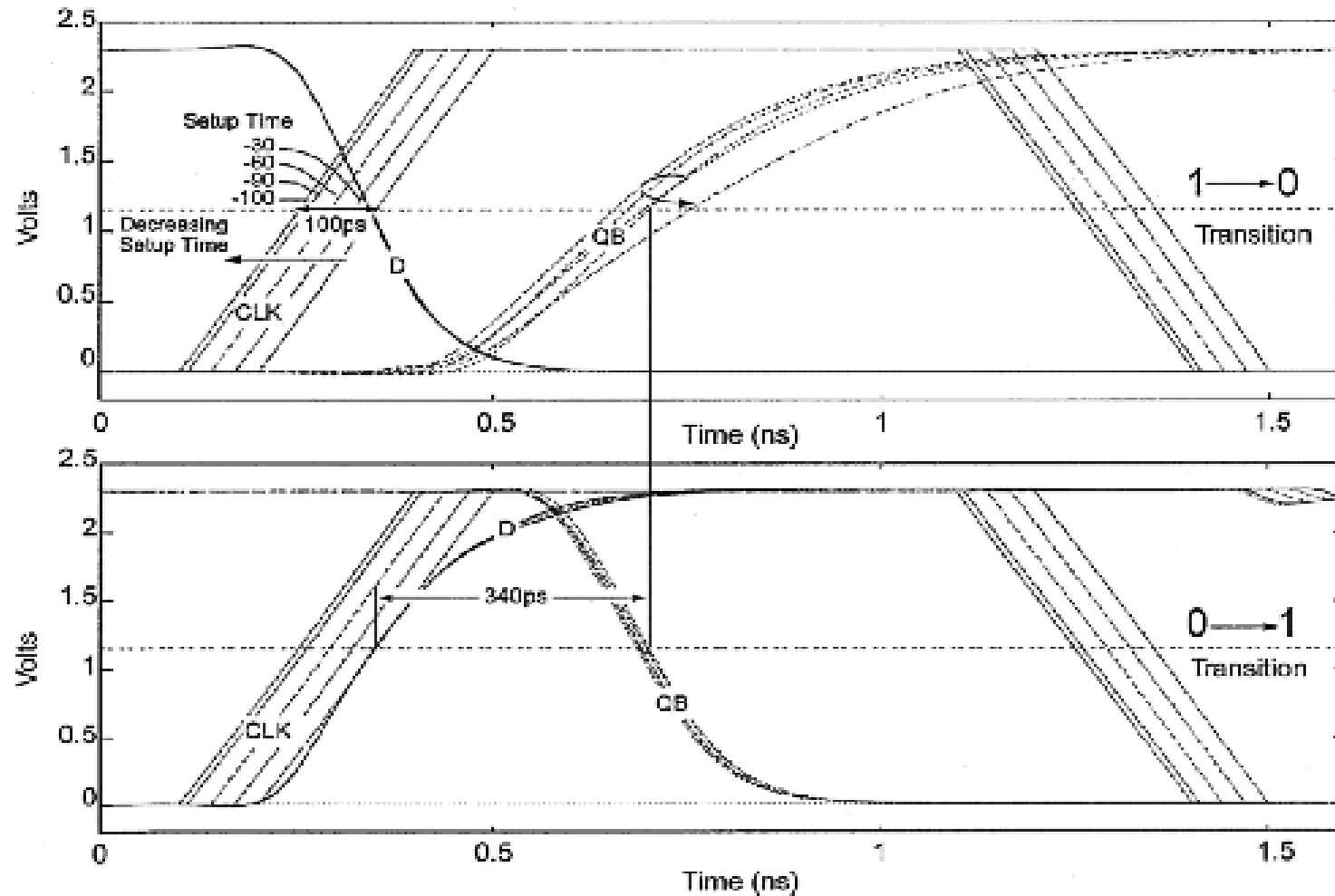

Partovi et al, ISSCC'96

Pulsed Latches

7474, from mid-1960's

 

Pulsed Latches


Sense-amplifier-based flip-flop, Matsui 1992.
DEC Alpha 21264, StrongARM 110

First stage is a sense amplifier, precharged to high, when $Clk = 0$


After rising edge of the clock sense amplifier generates the pulse on S or R

The pulse is captured in S-R latch

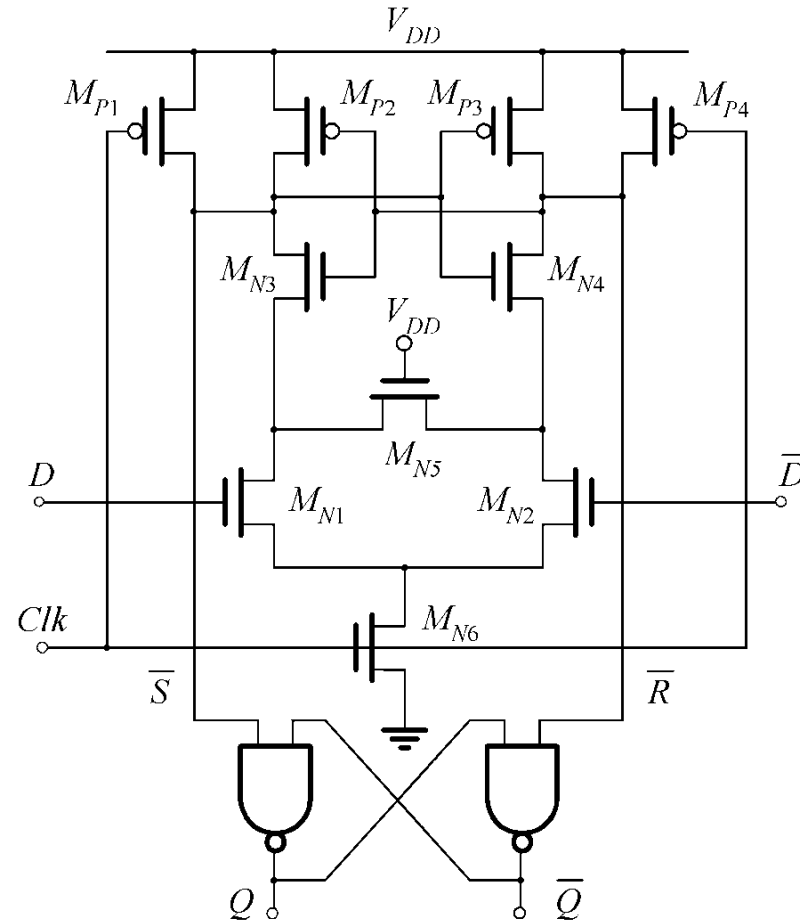
Cross-coupled NAND has different propagation delays of rising and falling edges



Sense Amplifier-Based Flip-Flop

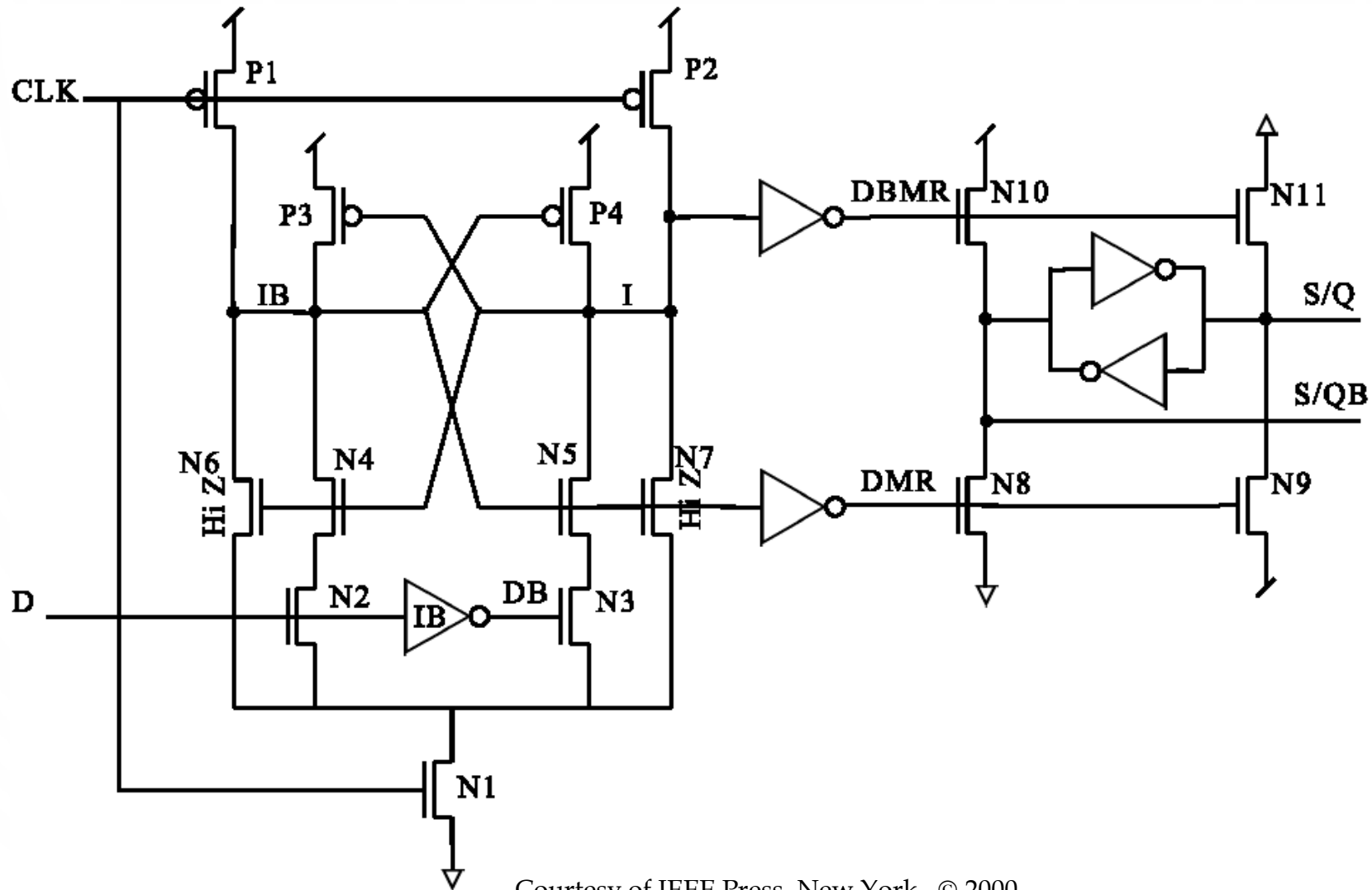

Sampling Window Comparison

 

Naffziger, JSSC 11/02

Summary

- Flip-flop-based (edge-triggered) timing dominates today
- Latch-based timing can increase performance, but needs extra care
- There is also asynchronous design
- Logical effort can be used to analyze latch timing

Next Lecture

- Variability