

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering and Computer Sciences**

**Jan M. Rabaey**

**Homework 2**

**NTU 6342 / EECS 241**  
**Spring 2007**

*Note: This is an individual assignment. For problem 1, please attach zoom-in plots from SPICE simulation, as well as the SPICE input files.*

**Due: February 16 (Friday) via email or post.**

### **1. Cell Library Design**

The AOI4 gate is a complex gate that finds wide use in today's standard cell library. Its functionality is defined by  $Z = -(AB + CD)$ .

- a. Design such a gate in static 65nm CMOS. Device sizes will be  $W_n/L_n = 0.18\mu\text{m}/65\text{nm}$ ,  $W_p/L_p = 0.36\mu\text{m}/65\text{nm}$ . Measure the energy, delay and energy-delay product. The cell inputs should be driven by unit inverters, the cell output should be loaded with 4 unit inverters to suppress overshoot.
- b. Redesign the same gate using DCVSL. Use the Karnaugh map technique to synthesize the complementary pull down networks, for which you will use NMOS devices sized as  $W_n/L_n = 0.18\mu\text{m}/65\text{nm}$ . Sweep the width of the PMOS cross-coupled load and plot delay, energy and energy-delay. What is the optimal width value from an energy perspective? What about energy-delay?
- c. Repeat part 2, but instead of using a cross-coupled load, put an inverter at the end of each chain, followed by a keeper with the gate tied to the inverter output.

### **2. Pulsed Static CMOS**

- a. Design a two-input XOR gate using the PS-CMOS logic style
- b. Size the gate for optimum performance using logical effort analysis. Assume that each device within a NAND or NOR gate has the same size.

### **3. Pass Transistor Logic**

Consider the circuit shown in Figure 1. Assume  $V_{Tn} = |V_{Tp}| = 300\text{mV}$ .

- a. Derive the minimum supply such that the circuit is still operational
- b. Determine the critical path, and give an expression for its delay.
- c. Discuss power dissipation of this circuit. Is there a problem?
- d. Propose two circuit modifications to improve the performance and power dissipation of the circuit, and discuss the pros and cons of each of them.
- e. What are the impacts on the performance and power consumption of this circuit if the threshold voltage of this process is lowered?

 


Figure 1: Circuit for problem 3.