

- a) Passband:  $f_c = 20 \text{ MHz}$        $R_p < 0.2 \text{ dB}$   
 Stopband:  $f_s = 35 \text{ MHz}$        $R_s < 65 \text{ dB}$


Using Matlab "ellipord":

$N = 6$        $\omega_n = 2\pi \cdot 20 \text{ Mrad/s}$

b) Reflection coeff:  $\rho = \sqrt{1 - 10^{-0.1 R_p}} = 21.2\%$   
 $\approx \underline{\underline{20\%}}$

Steepness Factor:  $\Delta\omega_s = \frac{f_s}{f_c} = 1.75$

Prototype: Williams p. 11.87

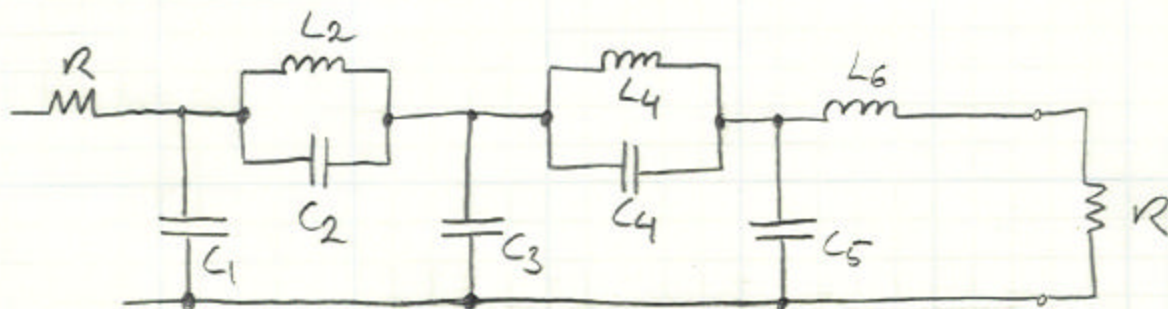

$\Delta\omega_s = 1.756$ ,  $A_{\min} = 67.8 \text{ dB} > 65 \text{ dB}$

$\Rightarrow$

$C_1 = 1.040$	$C_4 = 0.2063$
$C_2 = 0.1206$	$L_4 = 1.477$
$L_2 = 1.369$	$C_5 = 1.374$
$C_3 = 1.585$	$L_6 = 1.153$

Using Matlab:

Iterate R until denormalization yields reasonable capacitor values:

R = 10000

using:

-----  
Lr=R/Wn  
Cr=1/(R\*Wn)  
C1=C1n\*Cr  
C2=C2n\*Cr  
C3=C3n\*Cr  
C4=C4n\*Cr  
C5=C5n\*Cr  
L3=L3n\*Lr  
L4=L4n\*Lr  
L6=L6n\*Lr

Lr = 7.9577e-005

Cr = 7.9577e-013

denormalized component values:

-----

C1 = 8.2761e-013

C2 = 9.5970e-014

C3 = 1.2613e-012

C4 = 1.6417e-013


C5 = 1.0934e-012

L3 = 1.0894e-004


L4 = 1.1754e-004

L6 = 9.1753e-005

(c)

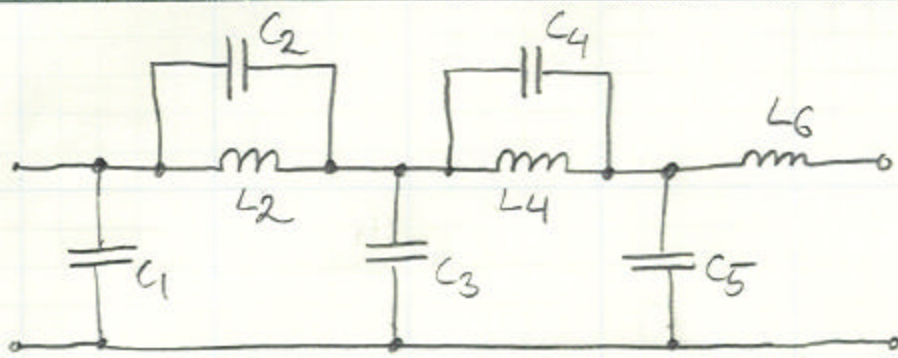

⇓ EQUIVALENT

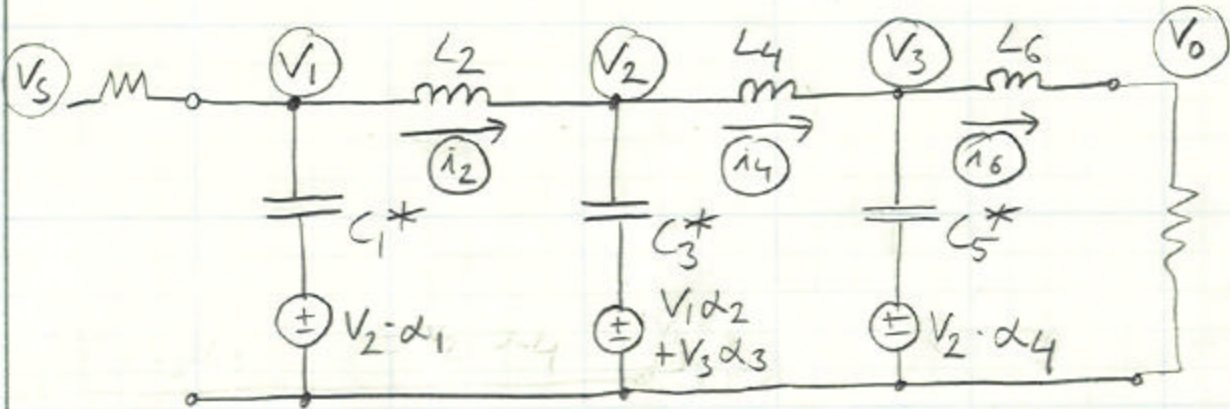

$$\alpha_1 = \frac{C_2}{C_1 + C_2}$$

$$C_1^* = C_1 + C_2$$

$$\alpha_2 = \frac{C_2}{C_3^*} \quad C_3^* = C_2 + C_3 + C_4$$

$$\alpha_3 = \frac{C_4}{C_3^*}$$

$$\alpha_4 = \frac{C_4}{C_4 + C_5}$$

$$C_5^* = C_4 + C_5$$

c)

$$V_1 = \frac{1}{sC_1^*} \left[ \frac{V_s - V_1}{R} - I_2 \right] + \alpha_1 V_2 \quad (1)$$

$$I_2 = \frac{1}{sL_2} [V_1 - V_2]$$

$$V_{I_2} = I_2 \cdot R^* = \frac{R^{*2}}{sL_2} \left[ \frac{V_1}{R^*} - \frac{V_2}{R^*} \right] \quad (2)$$

$$V_2 = \frac{1}{sC_3^*} [I_2 - I_4] + \alpha_2 V_1 + \alpha_3 V_3 \quad (3)$$

$$I_4 = \frac{1}{sL_4} [V_2 - V_3]$$

$$V_{I_4} = I_4 \cdot R^* = \frac{R^{*2}}{sL_4} \left[ \frac{V_2}{R^*} - \frac{V_3}{R^*} \right] \quad (4)$$

$$V_3 = \frac{1}{sC_5^*} [I_4 - I_6] + \alpha_4 V_2 \quad (5)$$

$$I_6 = \frac{1}{sL_6} [V_3 - V_0]$$

$$V_{I_6} = I_6 \cdot R^* = \frac{R^{*2}}{sL_6} \left[ \frac{V_3}{R^*} - \frac{V_0}{R^*} \right] \quad (6)$$

with:  $I_2 = \frac{V_{I_2}}{R^*}$


$$I_4 = \frac{V_{I_4}}{R^*}$$

$$I_6 = \frac{V_{I_6}}{R^*}$$


$$V_0 = I_6 \cdot R$$

$$= V_{I_6} \frac{R}{R^*}$$

c)

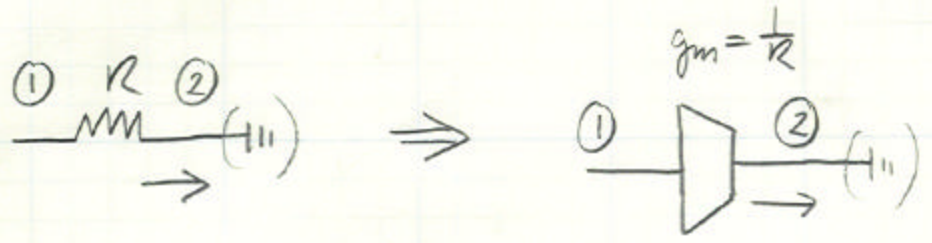

noise modelling:

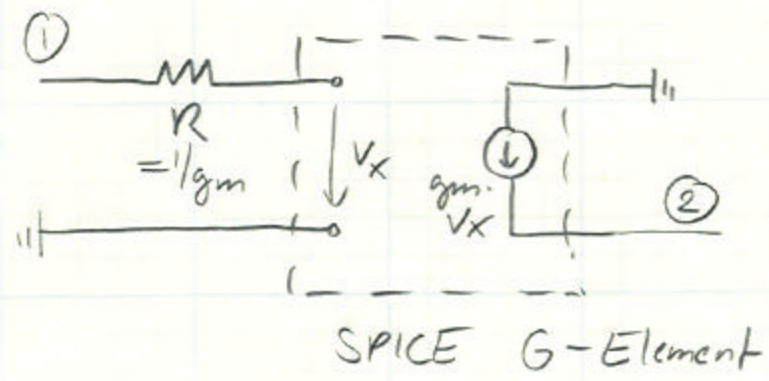


→ See attached schematic

$$G_m = \frac{1}{R}$$

$$G_m^* = \frac{1}{R^*}$$

d)

gain scaling:

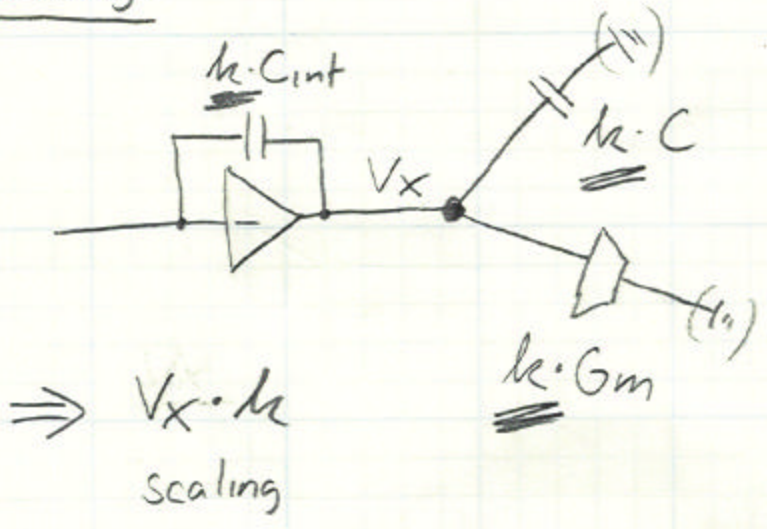

→ peak gain of unity from each integrator


→ See attached Plot ①

# Gm-C Implementation

$$G_m = \frac{1}{R}$$

$$G_m^* = \frac{1}{R^*}$$

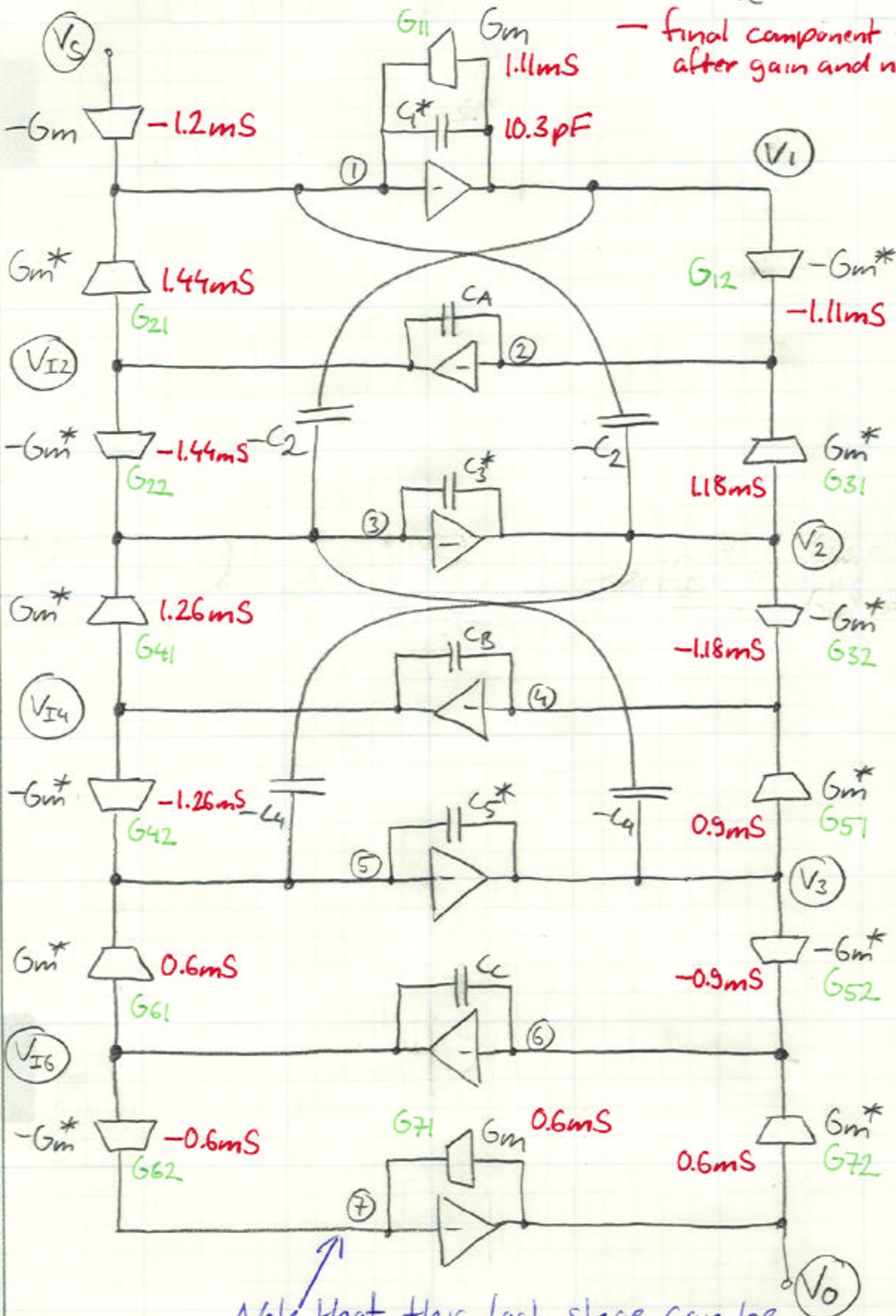- final component values after gain and noise scaling



Note that this last stage can be eliminated!  $\Rightarrow$  finite broadband noise

Component values for active circuit:

-----

using R\* = 10k and noise multiplier knoise = 12.04

Gm = 1.2040000000000000e-003  
G1 = 1.1125791600000000e-003  
G2 = 1.4424998200000000e-003  
G3 = 1.1800082000000000e-003  
G4 = 1.2642945000000000e-003  
G5 = 9.0186341000000001e-004  
G6 = 6.0204500000000001e-004  
G7 = 6.0204500000000001e-004


Cint1 = 1.027551560209852e-011  
Cint2 = 1.571481785937049e-011  
Cint3 = 1.795313656436392e-011  
Cint4 = 1.486000241283849e-011  
Cint5 = 1.134149859621723e-011  
Cint6 = 5.523932934198271e-012

$\Delta$ : v("vo" ?result "A"  $\diamond$ : v("vi6" ?result "  
 $\triangle$ : v("v2" ?result "A"  $\square$ : v("v3" ?result "A"  
 $\square$ : v("v1" ?result "A"

SPEC

Plot ①

Peak Stage  
Gains after  
scaling

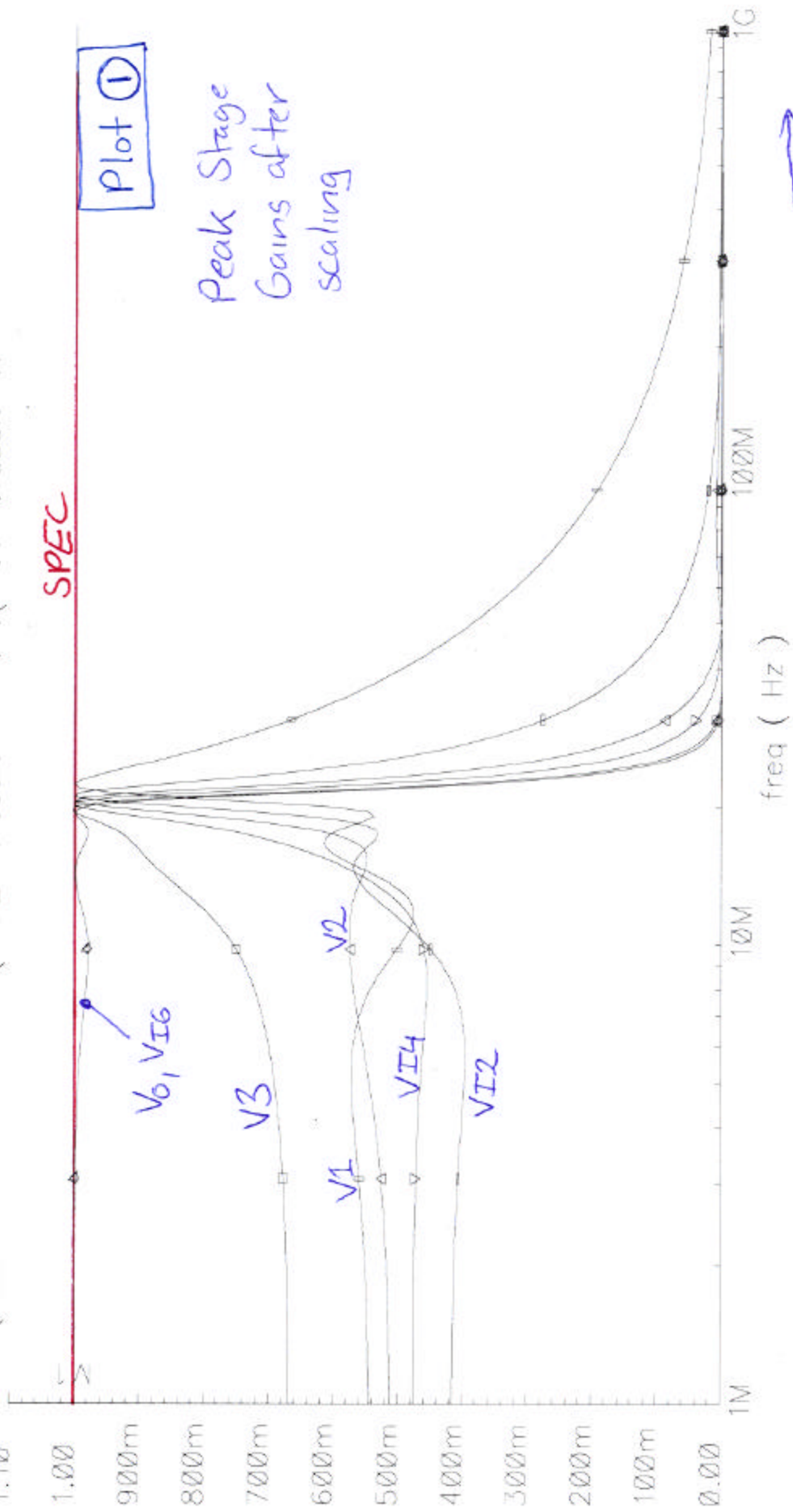

f

( )



d) ckt:

$$\underline{\text{Noise}}: \quad \sim \sqrt{\frac{kT}{C}}$$

all  $C \uparrow$  to reduce noise,

all  $G_m \uparrow$  to keep same xfer function

before scaling  $\sqrt{\int_0^{100\text{meg}} v_{on}^2 df} = 347 \mu\text{Vrms}$

$\Rightarrow$  introduce noise scaling factor

(3.47)  $k_{\text{noise}} = (3.47)^2$  to get

$$\sqrt{\int v_{on}^2 df} \stackrel{!}{=} 100 \mu\text{Vrms}$$

$\rightarrow$  Noise Integral Plot see attached (2)


$\rightarrow$  Frequency response see attached plots (3), (4)

$\Rightarrow$  exact match with  $\checkmark$

2x transfer function of passive LC ckt.

$\rightarrow$  scaled component values see above schematic
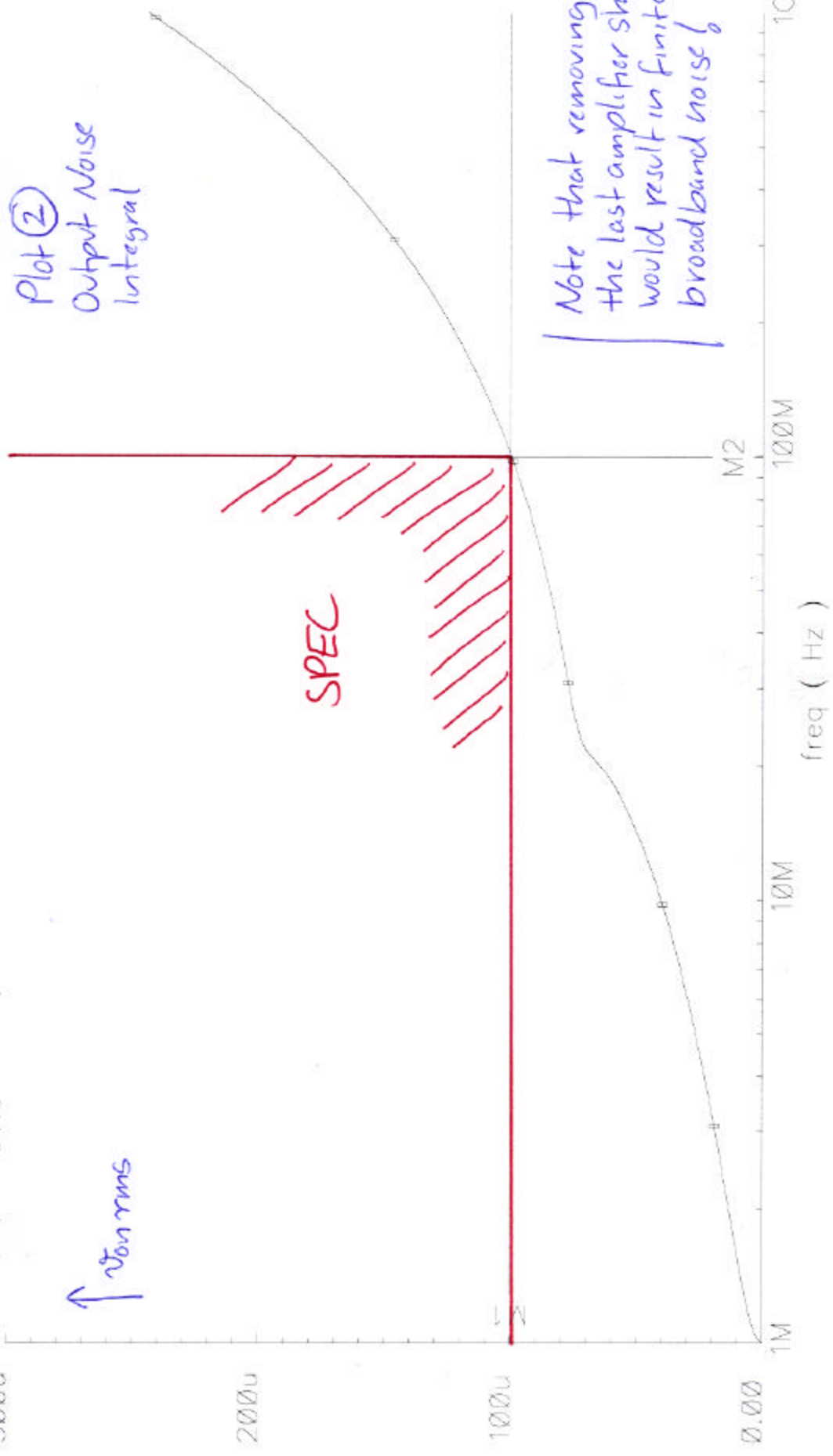
```
plot(sqrt(iinteg((getData("out") ?result "ONoise-noise" ?resultsDir "/home/bisc/b/boiser/b
```




A: (202.834M 433.912u) delta: (-102.834M -87.7573u)  
• B: (100M 346.154u) slope: 853.388f

```
-: dB20(((v "vop" ?result "ACSweep-ac" ?resultsDir "/home/bisc/b/bozer/bmurmann/ee247/hw") * 2)) Passive
: dB20((v "vo" ?result "ACSweep-ac" ?resultsDir "/home/bisc/b/bozer/bmurmann/ee247/hw")) Active
```

↑  $|H(f)|$  [dB]


Plot ③

SPEC

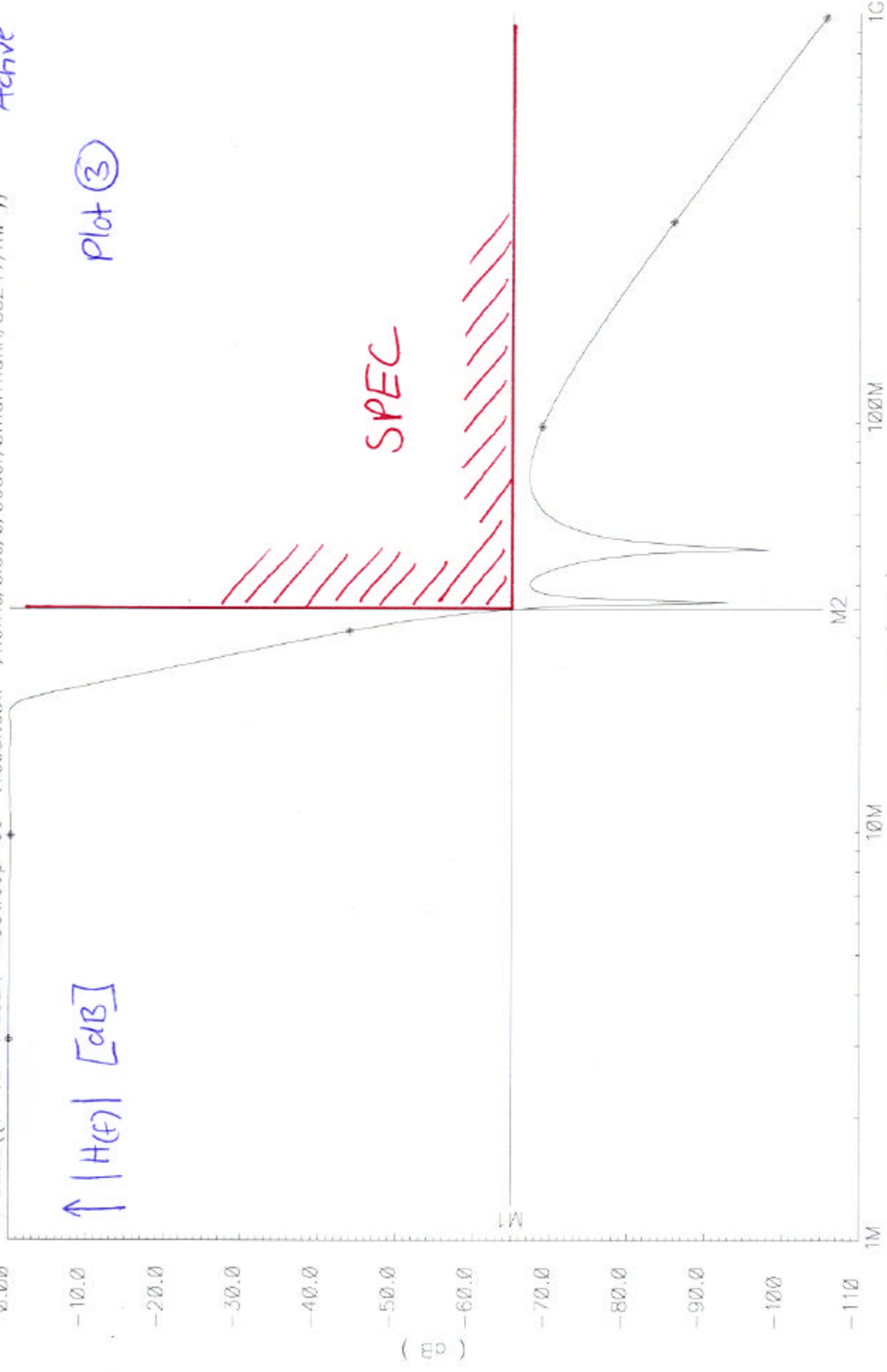


→ f

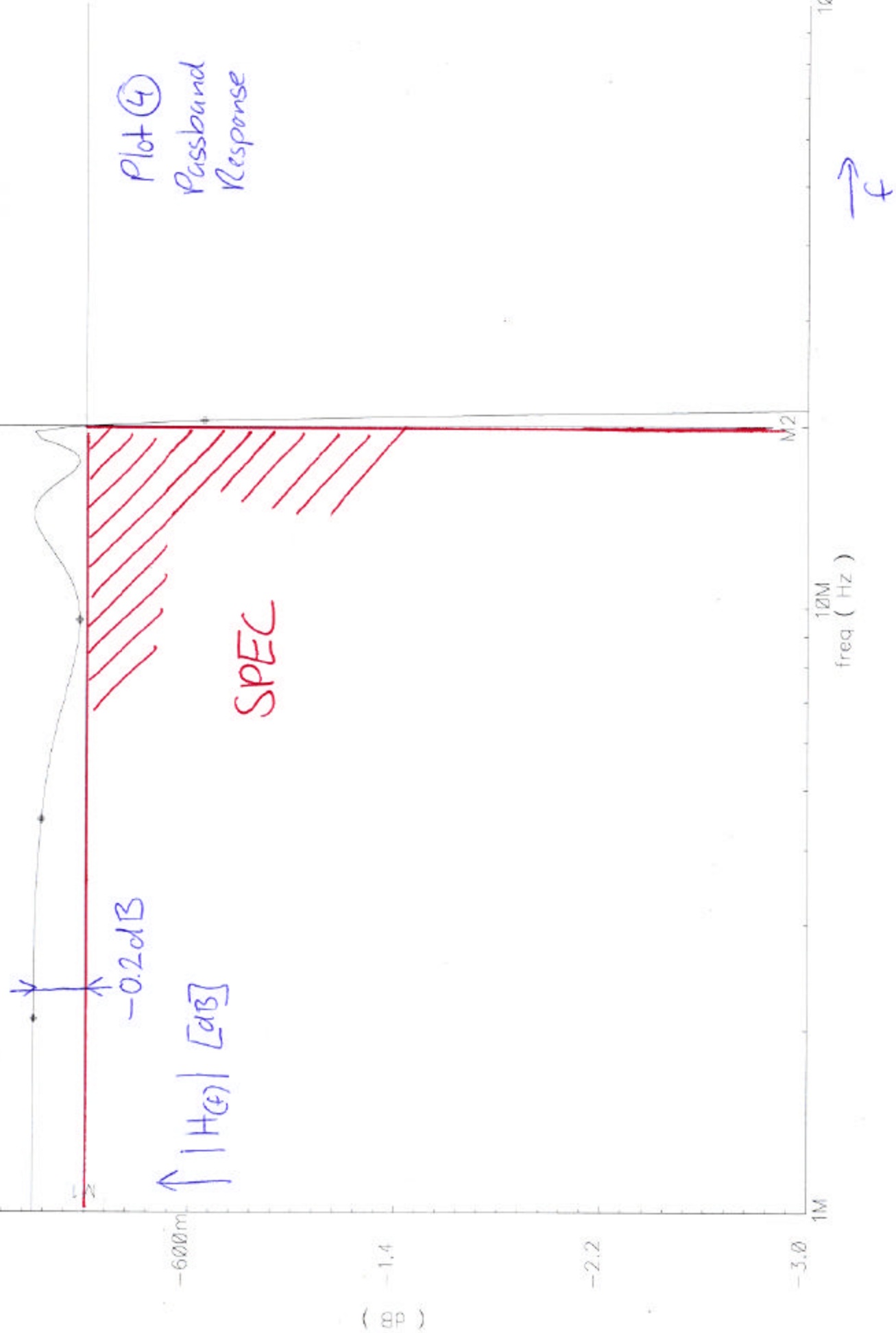-: dB20(((v "vop" ?result "ACSweep-ac" ?resultsDir "/home/bisc/b/boeser/bmurm/ee247/hw") \* 2)) **Passive**  
 : dB20(((v "vo" ?result "ACSweep-ac" ?resultsDir "/home/bisc/b/boeser/bmurm/ee247/hw")) **Active**




e)

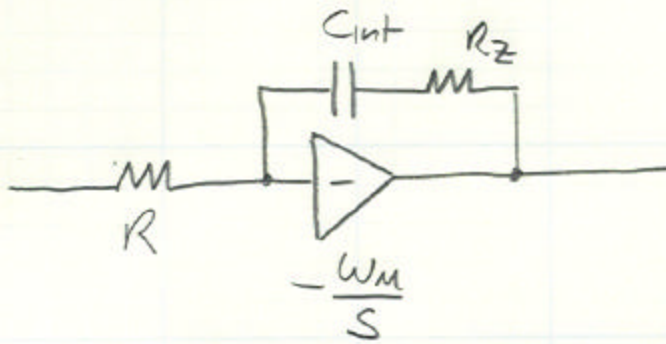

$$R_2 = \frac{1}{\omega_m C_{int}}$$

cancel parasitic pole in the above ckt.

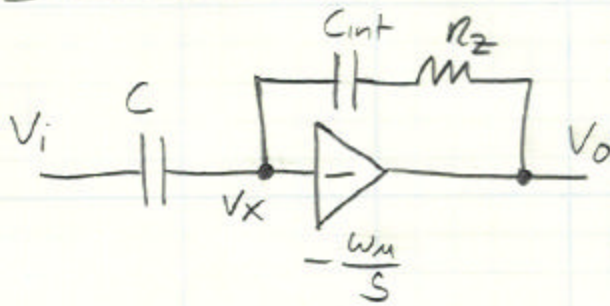

⇒  $R_2$  does not cancel  $f_{p2}$  for capacitive input branches!

$$0 = (V_i - V_x) sC + (V_o - V_x) \cdot \frac{1}{R_2 + \frac{1}{sC_{int}}}$$

$$V_x = - \frac{sV_o}{\omega_m}$$


$$0 = V_i sC + V_o \left( \frac{1 + \frac{s}{\omega_m}}{R_2 + \frac{1}{sC_{int}}} + \frac{s^2}{\omega_m} \right)$$

$$\frac{V_o}{V_i} = - \frac{sC}{\frac{1 + \frac{s}{\omega_m}}{R_2 + \frac{1}{sC_{int}}} + \frac{s^2}{\omega_m}}$$

$$\frac{V_o}{V_i} = - \frac{\frac{1}{sC_{int}} (1 + sC_{int}R_z)}{s^2 \frac{RC^2}{\omega_M} + \frac{s}{\omega_M} + \left(1 + \frac{C}{C_{int}}\right)}$$

⇒ not possible to cancel  
the two parasitic poles in  $D(s)$

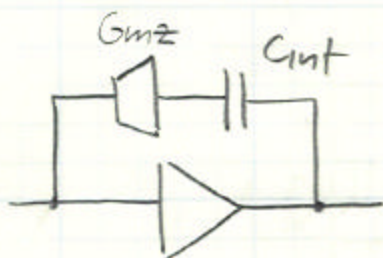⇒ Can not cancel completely in stages 1, 3, 5  
Cancel using:



$$G_{mz} = \frac{1}{R_z} = \omega_M \cdot C_{int}$$

Using Spice, found  $f_u > 4\text{GHz}$   
to meet Specs. → See plot ⑤  
(Passband Ripple critical to meet w/  
finite BW)

```
v: dB20((v "vo" ?result "ACSweep-ac" ?resuΔ: dB20((v "vo" ?result "ACSweep-ac" ?resu  
=: dB20((v "vo" ?result "ACSweep-ac" ?resuΔ: dB20((v "vo" ?result "ACSweep-ac" ?resu
```

$f_u = 46\text{Hz}$

Plot 5

$f_u = 500\text{MHz}$

SPEC

-0.2dB

$|H(f)|$  [dB]

0.0

-1.0

-2.0

-3.0

0.0000000

8.3333333M

16.666667M

25.000000M

freq ( Hz )

$f$

( dB )

M2

\* EE247 Homework#3 - Spectre Input - Boris Murmann

\*\*\*\*\* Circuit Description \*\*\*\*\*

simulator lang=spectre

parameters

```
+ R = 10k //*** Passive Network Components
+ C1 = 8.2761e-013
+ C2 = 9.5970e-014
+ C3 = 1.2613e-012
+ C4 = 1.6417e-013
+ C5 = 1.0934e-012
+ L2 = 1.0894e-004
+ L4 = 1.1754e-004
+ L6 = 9.1753e-005
+ knoise=3.47**2 //*** Noise Scaling Factor
+ k1=0.924 //*** Stage Amplitude Scaling Factors
+ k2=1.198
+ k3=0.98
+ k4=1.05
+ k5=0.749
+ k6=0.5
+ k7=0.5
+ Rx = 10k //*** Active Network Components
+ Gm = knoise*1/R
+ Gmx = knoise*1/Rx
+ C1x = knoise*(C1+C2)
+ C2x = knoise*C2
+ Ca = knoise*L2/Rx**2
+ C3x = knoise*(C2+C3+C4)
+ C4x = knoise*C4
+ Cb = knoise*L4/Rx**2
+ C5x = knoise*(C4+C5)
+ Cc = knoise*L6/Rx**2
+ G11 = k1*Gm
+ G12 = k1*Gmx
+ G2 = k2*Gmx
+ G3 = k3*Gmx
+ G4 = k4*Gmx
+ G5 = k5*Gmx
+ G6 = k6*Gmx
+ G7 = k7*Gmx
+ wu = 6.28*4Gig //*** Amplifier Unity Gain Frequency
```

\*\*\* Passive Ladder

```
Rs (vs n1) resistor r=R
C_1 (n1 0) capacitor c=C1
L_2 (n1 n2) inductor l=L2
C_2 (n1 n2) capacitor c=C2
C_3 (n2 0) capacitor c=C3
L_4 (n2 n3) inductor l=L4
C_4 (n2 n3) capacitor c=C4
C_5 (n3 0) capacitor c=C5
L_6 (n3 vop) inductor l=L6
Ro (vop 0) resistor r=R
```

\*\*\* Active Network

```
v_s (vs 0) vsource type=sine ampl=1 freq=1Meg mag=1
gin (vs 1) xcon g=-Gm
```



```

****
int1      (1 v1)      integz      Cint=k1*C1x wux=wu
g11      (v1 1)      xcon       g=G11
g21      (vi2 1)     xcon       g=G2
c21      (1 v2)      capacitor  c=-k3*C2x
c22      (3 v1)      capacitor  c=-k1*C2x
****
int2      (2 vi2)     integz      Cint=k2*Ca wux=wu
g12      (v1 2)     xcon       g=-G12
g31      (v2 2)     xcon       g=G3
****
int3      (3 v2)     integz      Cint=k3*C3x wux=wu
g22      (vi2 3)    xcon       g=-G2
g41      (vi4 3)    xcon       g=G4
c41      (5 v2)     capacitor  c=-k3*C4x
c42      (3 v3)     capacitor  c=-k5*C4x
****
int4      (4 vi4)     integz      Cint=k4*Cb wux=wu
g32      (v2 4)     xcon       g=-G3
g51      (v3 4)     xcon       g=G5
****
int5      (5 v3)     integz      Cint=k5*C5x wux=wu
g42      (vi4 5)    xcon       g=-G4
g61      (vi6 5)    xcon       g=G6
****
int6      (6 vi6)     integz      Cint=k6*Cc wux=wu
g52      (v3 6)     xcon       g=-G5
g72      (vo 6)     xcon       g=G7
****
amp7      (vo 0 7 0) vcvcs      gain=-1e6
g62      (vi6 7)     xcon       g=-G6
g71      (vo 7)      xcon       g=G7

```

```

subckt integz (vi vo)
  parameters Cint wux
  c1 (vo n1)      capacitor  c=Cint
  Rz (n1 vi)      resistor  r=1/(wux*Cint)
  k1 (vo 0 vi 0)  svcvcs  gain=-1 numer=[wux] denom=[0 1]
ends integz
subckt xcon (vi io)
  parameters g
  rn (vi vix)     resistor  r=1/g
  k1 (0 io vix 0) vccs  gm=g
ends xcon

```

\*\*\*\*\* Control Statements \*\*\*\*\*

```

SimOptions options
+   rawfmt=  psfbin
+   gmin=    1E-12
+   reltol=  1E-03
+   vabstol= 1E-06
+   iabstol= 1E-12
+   temp=    27
**+   currents= all

```

```

ACSweep  ac      start=1Meg stop=1Gig dec=100
ONoise   (vo 0)  noise start=1Meg stop=1Gig dec=100

```