

☞ Reference:H:\lib\Mathcad\defaults.mcd

NTU-EECS 247

Midterm Solution

Fall 2003

Boris Murmann

- 1) For an implementation with differentiators, we chose inductor voltages and capacitor currents as state variables

$$I_1 = sC_1(V_2 + V_o)$$

$$V_2 = sL_2\left(\frac{V_o}{R} + I_3\right)$$

$$I_3 = sC_3 \cdot V_o$$

Normalize: $V_1 = I_1 \cdot R$ $V_3 = I_3 \cdot R$ $C_2 = \frac{L_2}{R^2}$

$$V_1 = sRC_1(V_2 + V_o)$$

$$V_2 = sRC_2(V_o + V_3) \quad (\text{Note that } V_o \text{ is not the same as } V_3\dots)$$


$$V_3 = sRC_3 \cdot V_o$$

Where is the input??? Use KVL, KCL to get:


$$V_o = \frac{1}{2} \cdot (V_1 - V_1 - V_2 - V_3)$$

Circuit Diagram:

(Looks quite interesting...)

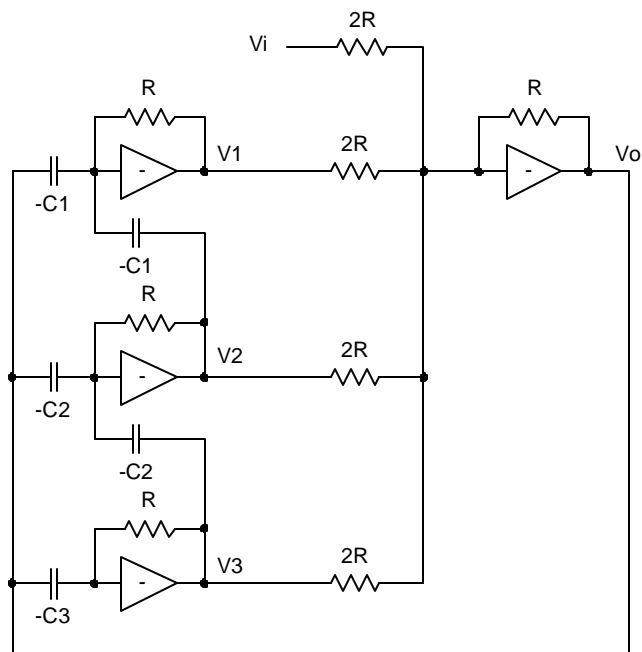

After gain scaling:

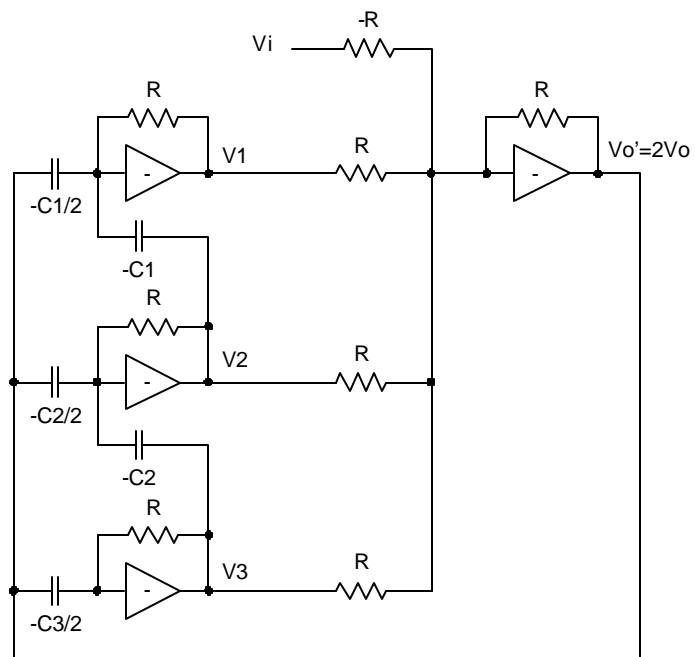

2) Worst case alias frequency: $f_a = f_s - 1\text{MHz}$

For greater 60dB attenuation:
(One frequency decade) $f_a > 10 \cdot 1\text{MHz}$

$$f_s - 1\text{MHz} > 10\text{MHz}$$

$$\boxed{f_s > 11\text{MHz}}$$

3) $f_{\text{out}} = 1.25f_s - f_s$ $\boxed{f_{\text{out}} = 0.25f_s}$

$$H(s) = \frac{RCs}{1 + 2RCs}$$

$$A_{\text{out}} = A \left| H(j \cdot 2\pi \cdot f_{\text{out}}) \right|$$

$$\boxed{A_{\text{out}} = A \cdot \frac{RC \cdot 2\pi f_{\text{out}}}{\sqrt{1 + (2RC \cdot 2\pi f_{\text{out}})^2}}}$$

4) Every other code missing - this is the same as a 9-bit ADC, so

$$\text{SNR} := 6.02 \cdot 9 + 1.76 \quad \boxed{\text{SNR} = 55.94} \text{ [dB]}$$

5) Phase1: $Q = V_1 \cdot (C_a + C_b)$

Phase2: $Q = V_o \cdot C_a + V_2 \cdot C_b$

$$Q = V_1 \cdot (C_a + C_b) \left| \begin{array}{l} \text{substitute, } Q = V_o \cdot C_a + V_2 \cdot C_b \\ \text{solve, } V_o \end{array} \right. \rightarrow \frac{(-V_2 \cdot C_b + V_1 \cdot C_a + V_1 \cdot C_b)}{C_a}$$

$$\boxed{V_o(z) = V_1 \cdot \left(1 + \frac{C_b}{C_a} \right) \cdot z^{-1} - V_2 \cdot \frac{C_b}{C_a}}$$