 



# Sampling

## Ideal Sampling



- Grab exact value of  $V_{in}$  when switch opens

## Practical Sampling

 

- $kT/C$  noise
- Finite  $R_{sw} \rightarrow$  limited bandwidth
- $R_{sw} = f(V_{in}) \rightarrow$  distortion
- Switch charge injection (EE240)
- Clock jitter

# $kT/C$ Noise

$$\frac{k_B T}{C} \leq \frac{\Delta^2}{12}$$

$$C \geq 12k_B T \left( \frac{2^B - 1}{V_{FS}} \right)^2$$


In high resolution ADCs  $kT/C$  noise usually dominates overall error (power dissipation argument).

B	$C_{min}$ ( $V_{FS} = 1V$ )
8	0.003 pF
12	0.8 pF
14	13 pF
16	206 pF
20	52,800 pF

# Acquisition Bandwidth

- The resistance  $R$  of switch  $S1$  turns the sampling network into a lowpass filter with risetime =  $RC = \tau$
- Assuming  $V_{in}$  is constant during the sampling period and  $C$  is initially discharged (a good idea—why?):

$$v_{out}(t) = v_{in}(1 - e^{-t/\tau})$$

 

# Switch On-Resistance

$$v_{in} - v_{out} \left( t = \frac{1}{2f_s} \right) \ll \Delta$$

$$v_{in} e^{-1/2f_s t} \ll \Delta$$

Worst Case:  $v_{in} = V_{FS}$


$$t \ll -\frac{T}{2 \ln(2^B - 1)}$$

$$R \ll -\frac{1}{2f_s C \ln(2^B - 1)}$$

## Example:

$B = 14$ ,  $C = 13\text{pF}$ ,  $f_s = 100\text{MHz}$

$T/\tau \gg 19.4$ ,  $R \ll 40\Omega$

 

# Switch On-Resistance

$$I_{D(\text{triode})} = \mathbf{mC}_{ox} \frac{W}{L} \left( V_{GS} - V_{TH} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\frac{1}{R_{ON}} \equiv \left. \frac{dI_{D(\text{triode})}}{dV_{DS}} \right|_{V_{DS} \rightarrow 0}$$

$$= \frac{1}{\mathbf{mC}_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$


$$= \frac{1}{\mathbf{mC}_{ox} \frac{W}{L} (V_{DD} - V_{TH} - v_{in})}$$

$$= \frac{1}{R_o} \frac{1}{1 - \frac{v_{in}}{V_{DD} - V_{TH}}} \quad \text{with} \quad R_o = \frac{1}{\mathbf{mC}_{ox} \frac{W}{L} (V_{DD} - V_{TH})}$$

$$R_{ON} = R_o \left( 1 - \frac{v_{in}}{V_{DD} - V_{TH}} \right)$$
 
# Sampling Distortion

$$v_{out} = v_{in} \left( 1 - e^{-\frac{T}{2\tau} \left( 1 - \frac{v_{in}}{V_{DD} - V_{TH}} \right)} \right)$$




$$T/\tau = 10$$

$$V_{DD} - V_{TH} = 2V \quad V_{FS} = 1V$$
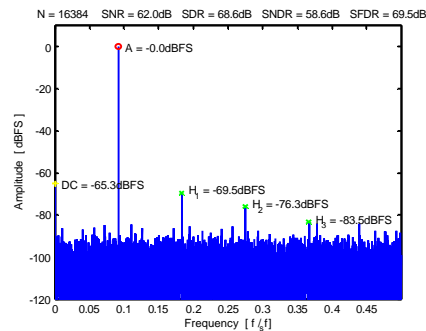
# Sampling Distortion

- SFDR is very sensitive to sampling distortion
- Solutions:
  - Overdesign switches
    - increased switch charge injection
  - Complementary switch
  - Maximize  $V_{DD}/V_{FS}$ 
    - increased noise
  - Constant  $V_{GS}$  ?  $f(V_{in})$ 
    - ...




$$T/\tau = 20$$

$$V_{DD} - V_{TH} = 2V \quad V_{FS} = 1V$$




# Constant $V_{GS}$ Sampling

 


- Switch overdrive voltage is independent of signal
- Error from finite  $R_{ON}$  is linear (to first order)



# Constant $V_{GS}$ Sampling

 


# Constant $V_{GS}$ Sampling Circuit

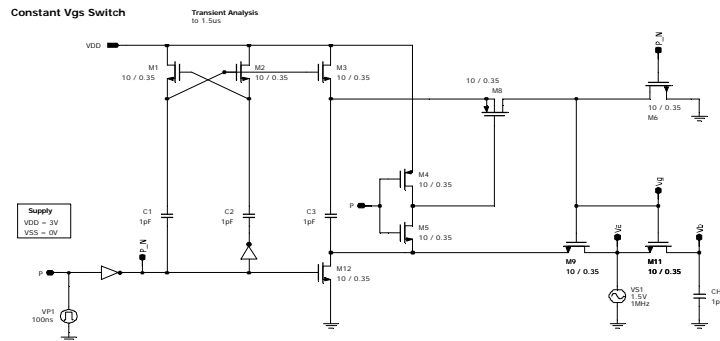


# Clock Multiplier

## Clock Booster

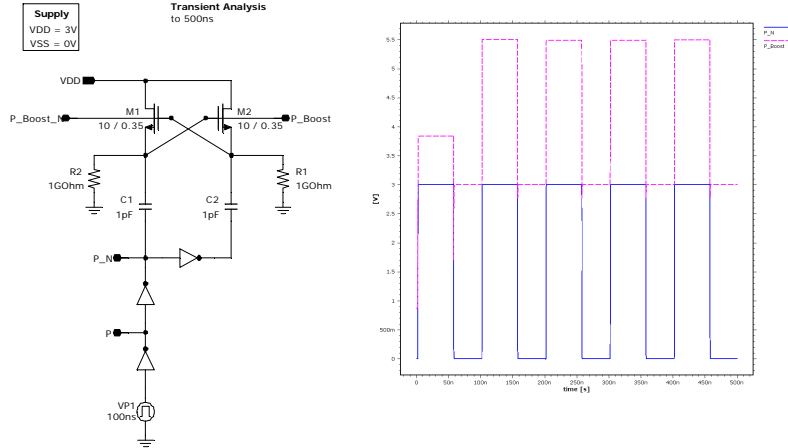


# Constant $V_{GS}$ Sampler: $\Phi$ LOW

## Constant $V_{GS}$ Switch: P is LOW

 


- Sampling switch M11 is OFF
- C3 charged to VDD

# Constant $V_{GS}$ Sampler: $\Phi$ HIGH

 


- C3 previously charged to VDD
- M8 & M9 are on: C3 across G-S of M11
- M11 on with constant  $V_{GS} = V_{DD}$

# Constant $V_{GS}$ Sampling

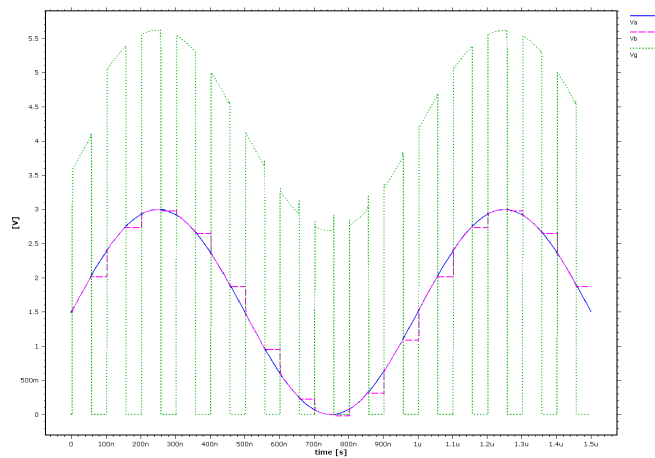


# Complete Circuit

 


Ref: A. Abo et al, "A 1.5-V, 10-bit, 14.3-MS/s CMOS Pipeline Analog-to-Digital Converter," JSSC May 1999, pp. 599.

# CMOS Sample & Hold

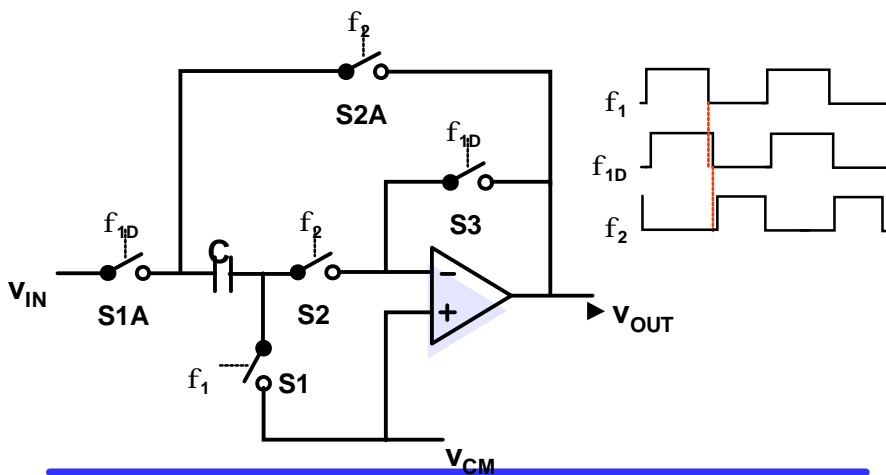





# CMOS Sample & Hold

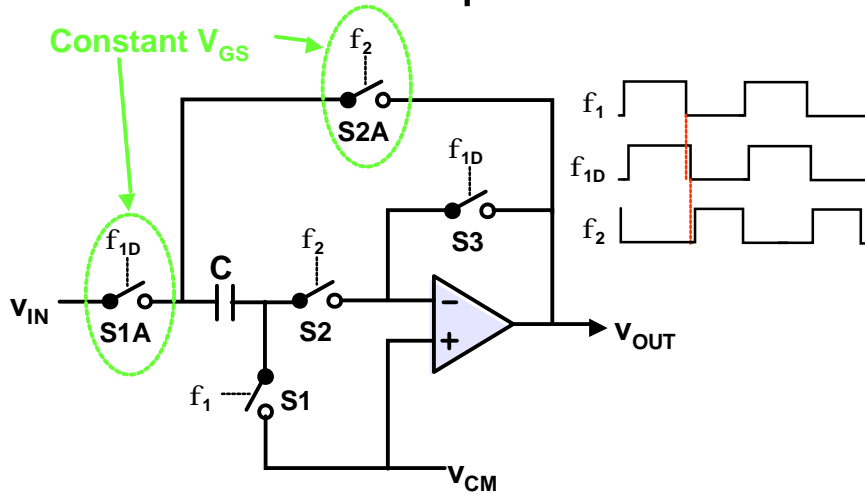

# CMOS Sample & Hold

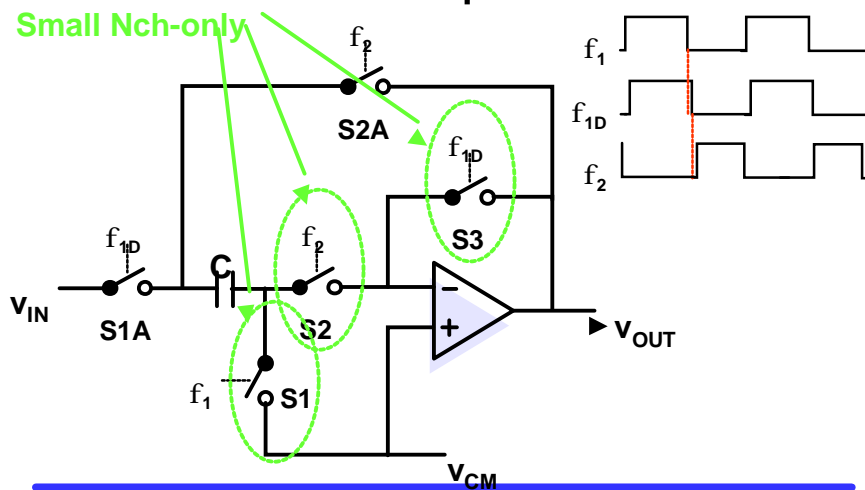

# CMOS Sample & Hold

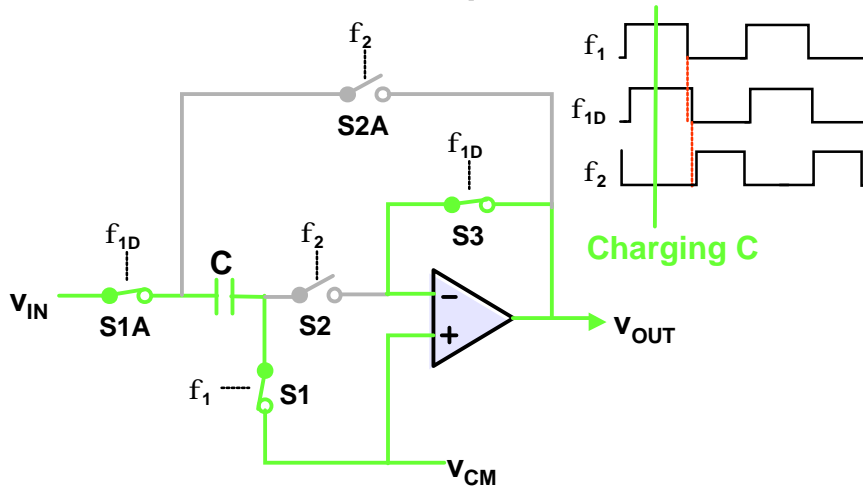


# CMOS Sample & Hold

- S1 is an n-channel MOSFET
- S1 provides as much of the sampling path resistance as possible ( $R=R_{S1A}+R_{S1}$ )
  - S1A is a wide (much lower resistance than S1) constant  $V_{GS}$  switch
  - If S1A's resistance is negligible, aperture delay depends only on S1 resistance
  - S1 resistance is independent of  $v_{IN}$ ; hence, aperture delay is independent of  $v_{IN}$

# Charge Injection

- At the instant of sampling, some of the charge stored in sampling switch  $S1$  is dumped onto  $C$ 
  - This unwanted charge is called “charge injection”
- The circuit on slide 15.2 has charge injection that varies in a wildly nonlinear fashion with  $v_{IN}$
- With the CMOS Sampling Circuit, charge injection comes only from  $S1$  and is first-order independent of  $v_{IN}$ 
  - Only a dc offset is added to the input signal
  - This dc offset can be removed with a differential architecture


# CMOS Sample & Hold

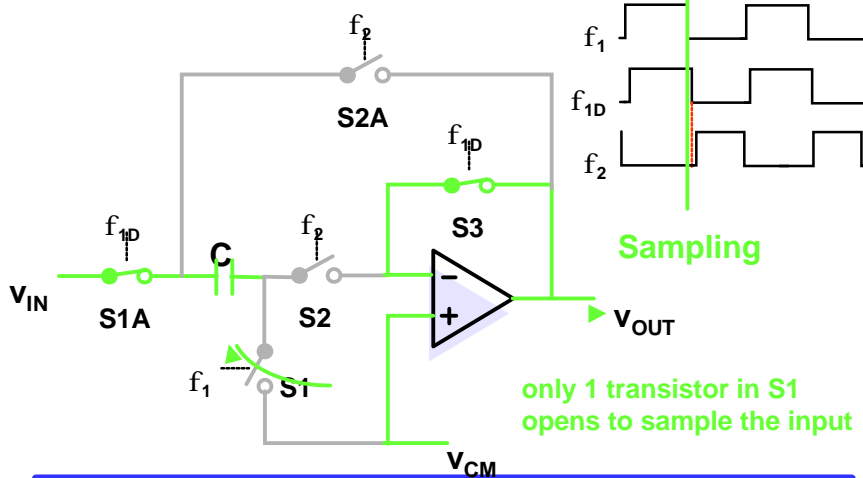

# CMOS Sample & Hold

- During  $\phi_2$ , the opamp buffers the sampling capacitor for loads that need it
- The hold topology is shown on the following slide...

# CMOS Sample & Hold

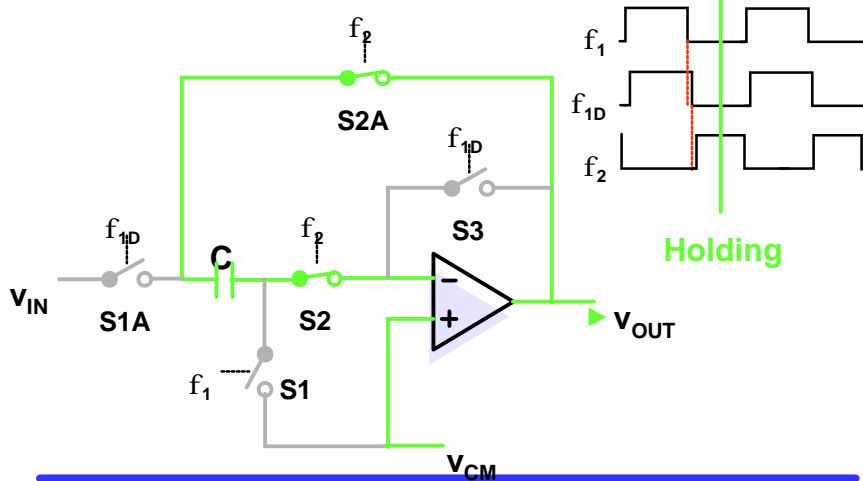


# Jitter

- All of the preceding analyses assume that sampling impulses are spaced evenly in time
- In the real world, separation of sampling impulses has some distribution around the nominal value  $T$
- The variability in  $T$  is called jitter

 
# Jitter

- The dominant cause of clock jitter in most chips is power supply noise produced by unrelated activity in other parts of the chip
- The inverter symbol represents a chain of gates in the sampling clock path



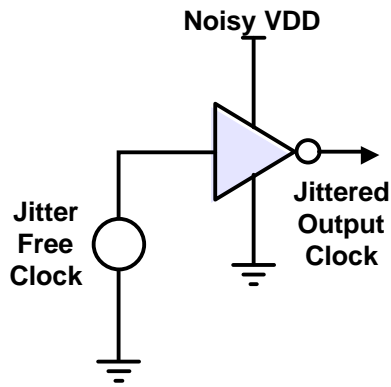
# Jitter

- Let's assume the inverter delay is 100psec, and that the delay varies by 20% per volt change in VDD (20psec/V)
- 200mV of power supply noise becomes 4psec of clock jitter


 
# Jitter


- Sampling jitter adds an error voltage proportional to the product of  $(t_J - t_0)$  and the derivative of the input signal at the sampling instant
- Jitter doesn't matter when sampling dc signals



# Jitter

- The error voltage is

$$e = x'(t_0)(t_j - t_0)$$

 

# Jitter Example

Sinusoidal input

Amplitude:  $A$   
 Frequency:  $f_x$   
 Jitter:  $?t$

$$x(t) = A \sin(2\pi f_x t)$$

$$x'(t) = 2\pi f_x A \cos(2\pi f_x t)$$

$$|x'(t)| \leq 2\pi f_x A$$

$$|e(t)| \leq |x'(t)| ?t$$

Worst case

$$A = A_{FS}$$

$$f_x = f_s / 2$$

$$|e(t)| \ll \frac{\Delta}{2} \cong \frac{A_{FS}}{2^{B+1}}$$

$$?t \ll \frac{1}{2^B \pi f_s}$$

B	$f_s$	$\Delta t \ll$ than
16	10 MHz	0.5 ps
12	100 MHz	0.8 ps
8	1000 MHz	1.2 ps

# The Jitter Law

- The worst case looks pretty stringent ... what about the “average”?
- Let's calculate the mean squared jitter error (variance)
- If we're sampling a sinusoidal signal
$$x(t) = A\sin(2\pi f_x t),$$
then
  - $x'(t) = 2\pi f_x A\cos(2\pi f_x t)$
  - $E\{[x'(t)]^2\} = 2\pi^2 f_x^2 A^2$
- If jitter is uniformly distributed from  $-\tau/2$  to  $+\tau/2$ 
  - $E\{(t_j - t_0)^2\} = \tau^2/12$

# The Jitter Law

- If  $x'(t)$  and the jitter are independent
  - $E\{[x'(t)(t_j - t_0)]^2\} = E\{[x'(t)]^2\} E\{(t_j - t_0)^2\}$

- Hence, the jitter error power is

$$E\{e^2\} = p^2 f_x^2 A^2 \tau^2 / 6$$

- If the jitter is uncorrelated from sample to sample, this “jitter noise” is white



# The Jitter Law

$$\begin{aligned}DR_{\text{jitter}} &= \frac{A^2/2}{p^2 f_x^2 A^2 t^2 / 6} \\ &= \frac{3}{p^2 f_x^2 t^2} \\ &= -20 \log_{10}(f_x t) - 5.172 \text{dB}\end{aligned}$$

$f_x$	$\tau$	$DR_{\text{jitter}}$	ENOB
1 MHz	1 ns	55 dB	8.8
1 MHz	2 ps	109 dB	17.8
100 MHz	0.4 ps	83 dB	13.5
1000 MHz	0.5 ps	61 dB	9.8

# The Jitter Law

- The Jitter Law must be respected whenever you require high-resolution conversion of high frequency signals
  - Sampling a 1MHz signal with 1nsec of peak-to-peak jitter yields a dynamic range of only 55dB
- In practice, jitter is usually controlled to add negligible to the total converter error (i.e. thermal and quantization noise)
- This translates into the jitter being ~10dB below other noise sources
  - For 16 Bit conversion of 1MHz signals, a -109dB jitter DR limit requires < 2 psec peak-to-peak jitter

# The Jitter Law

- Clock jitter in the single-digit picosecond range doesn't just happen
  - Separate supplies
  - Separate analog and digital clocks
  - Short inverter chains between clock and sampling switch
- Few, if any, other analog-to-digital conversion nonidealities have the same symptoms as sampling jitter:
  - RMS noise proportional to input frequency
  - RMS noise proportional to input amplitude
- So, if sampling clock jitter is limiting your dynamic range, it's easy to tell, but difficult to fix
  - Very difficult to fix in silicon without all-layer mask revisions