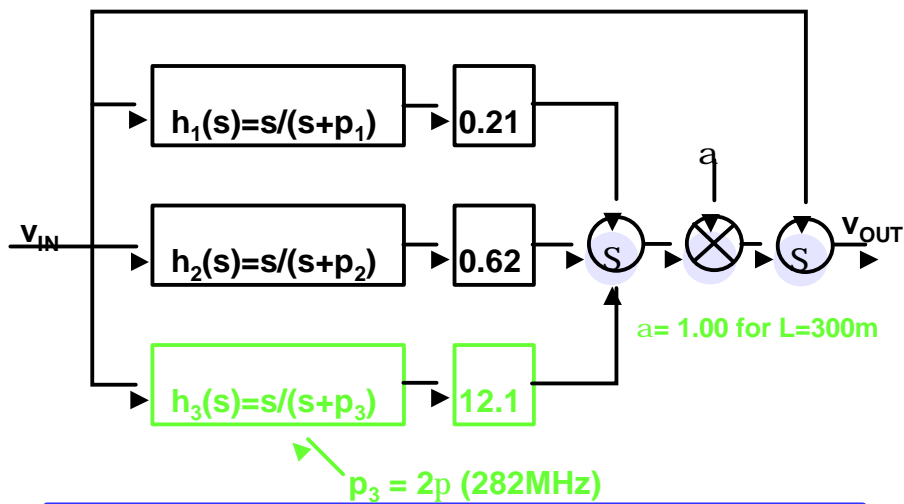


Offset Control

- Offset control in data receivers
 - dc offset
 - ac coupling
 - Baseline wander
 - Quantized feedback
- Decision circuits


Equalizer Gain



Equalizer Gain

- Comlinear's cable equalizer uses 2 of the 3-pole sections in cascade
 - the highest value of equalizer gain appears to approach $12.1^2=43\text{dB}$ at high frequencies
- In practice, equalizer bandlimiting is required to limit noise and achieve acceptable bit error rates
 - maximum equalizer gain falls to about 32dB ...

300m Equalizer Response

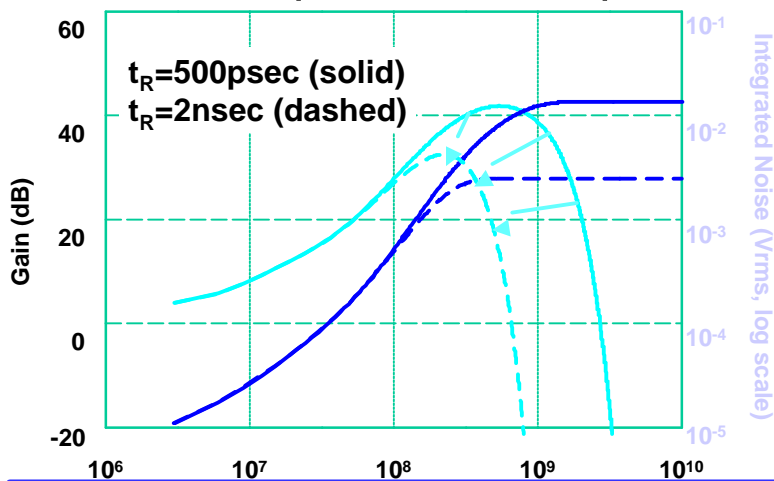


Equalizer Offsets

- Almost all data equalizers provide gain to compensate for channel losses
 - This gain also gains up offsets arising from device mismatches in amplifier stages
 - Typical high-speed amplifier stages have $\sim 10\text{mV}$ input-referred offsets
- Most implementations of the Comlinear equalizer provide that gain (43dB) also to dc offsets
 - Left uncorrected, a 10mV input-referred offset becomes a 1.5V output offset ...




Offset Eye Diagrams

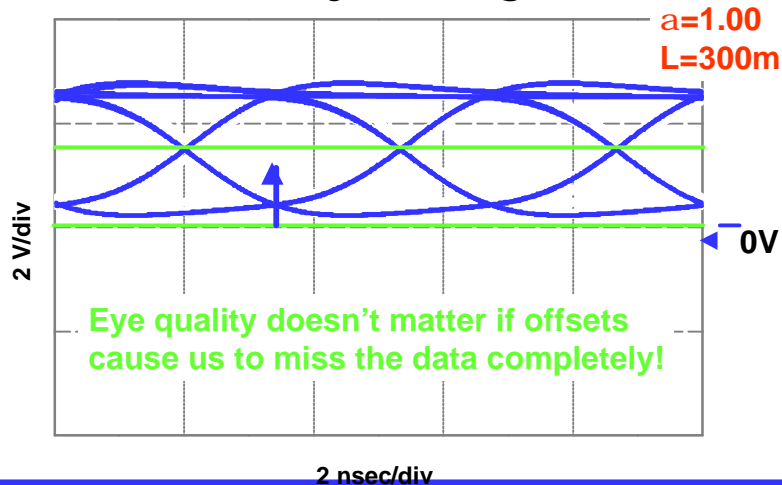

Equalizer Offsets

- Even modest offsets can reduce the effective eye opening significantly
- The resulting effect on P_E can be severe
- The offset in the next slide results in a substantial bias in favor of -1→+1 errors ...

Offset Eye Diagrams

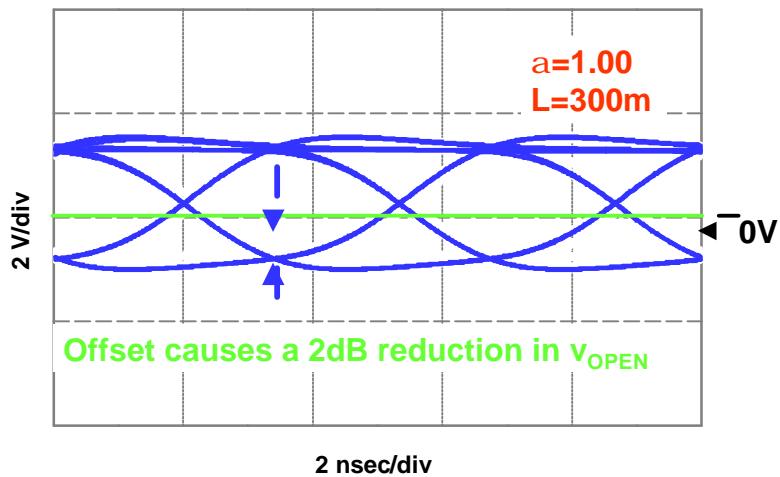

Equalizer Offsets


- Offset control is an important and under-appreciated component of data receiver architecture
 - The catch is that offsets must be controlled without slowing down the signal path
 - Offset control schemes often take as much design time as equalization itself
 - Initial design schedules typically underestimate this effort by wide margins

ac Coupling


- ac coupling between amplifier stages is an obvious form of offset control:

$$H(s) = \frac{s}{s + \omega_p}$$

- Where should we set the HPF corner frequency?

 

Comlinear 3-Pole Section

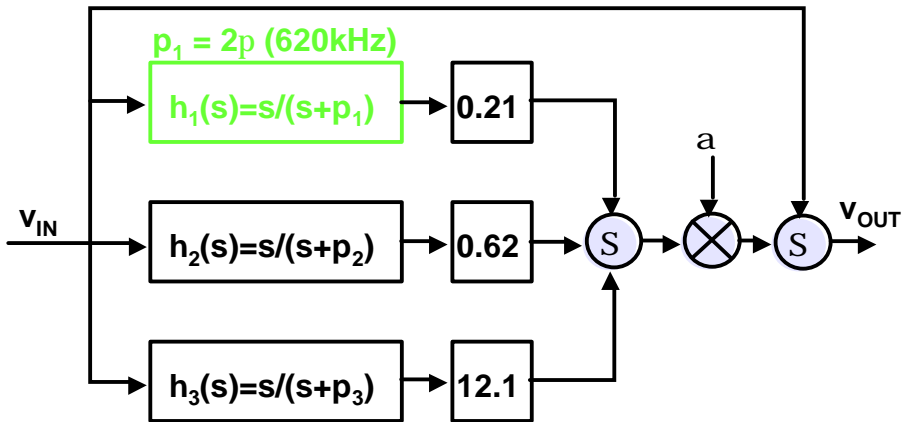


phase equalization provided by p_1 ends below 62kHz

ac Coupling

- A $10M\Omega$, $2.5pF$ ac coupling network ($\tau=RC=25\mu\text{sec}$) can remove dc offsets from the Comlinear equalizer without much effect on its phase response above 62kHz
 - The large "resistor" can be realized with a long, narrow FET
- Does the high pass filter's own frequency response create any new problems in the NRZ data receiver?
 - The answer is "yes"
 - The problem is called "baseline wander"


Baseline Wander

 - Suppose our NRZ data stream comes from a sparsely populated binary file with lots of consecutive zeros in it
- We'll model the data stream as
 - 100 μ sec of random $\pm 1V$ data at 300Mb/s
 - 100 μ sec of a fixed $-1V$ level (models 30000 zeros in a row)




$$H(s) = \frac{s}{s + \omega_p}$$

Sparse HPF Input Data

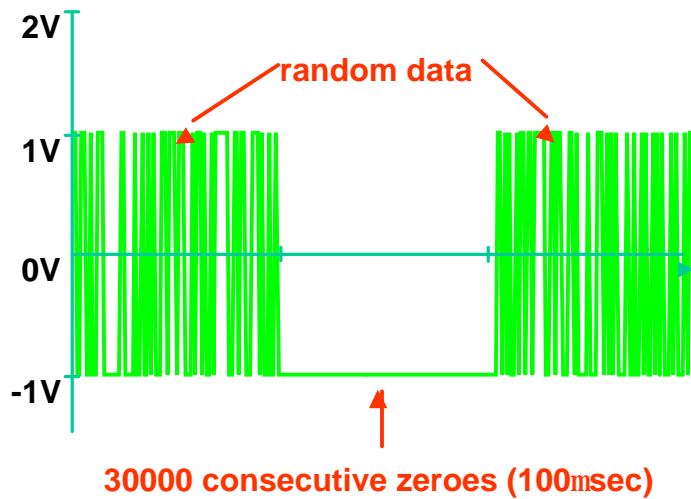

HPF Output

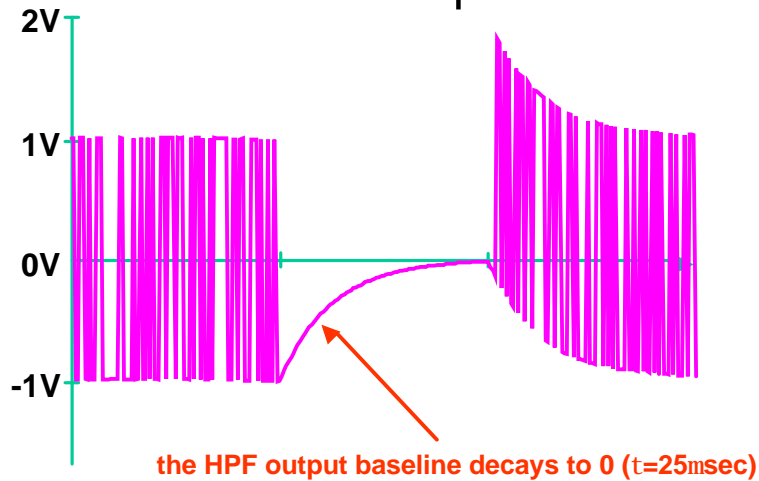

Baseline Wander

- The high pass filter causes the middle of the data eye to wander with low frequency components in the NRZ data stream
 - Common data idling patterns move decision thresholds to the edges of the data eye
 - With disastrous consequences for bit error rates
 - Localized concentrations of -1 's or $+1$'s lasting on the order of 0.05τ reduce eye opening 0.5dB
 - Substantially increasing bit error rates
- What can we do about it?

Baseline Wander

- Data scrambling can reduce the probability of perverse patterns
 - Common sparse sequences are mapped to transition-rich sequences
 - With 1:1 mapping, some irregular sequence will still map to a perverse baseline sequence, and the resulting baseline wander will cause errors
- Coding tricks can add extra bits to the data stream to ensure transition density
 - An 8b-9b code maps 8 data bits to 9 transmitted bits, with sparse patterns omitted from the 9b patterns
 - NRZ data throughput is reduced by the 8/9 factor




Quantized Feedback

- The problem is that the HPF assumes the data sequence has zero mean
- If we knew the data sequence, we could of course calculate this mean and add it to the HPF output
- Do we?
 - It appears at the output of the receiver ...




Quantized Feedback

 - Quantized feedback combines a decision circuit (a comparator) and an ac coupling network in an ingenious way [2]:



Quantized Feedback

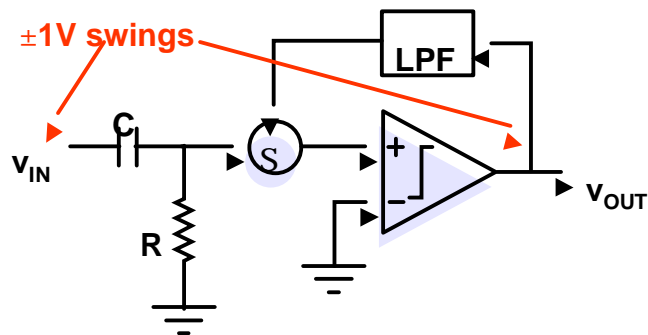
- The comparator is designed to produce the same p-p output swing as v_{IN} :



Quantized Feedback


- How should we set the bandwidth of the LPF?
 - Model the quantizer as a gain (=1)
 - We want $V_{OUT} = V_{IN}$
 - Solve ...
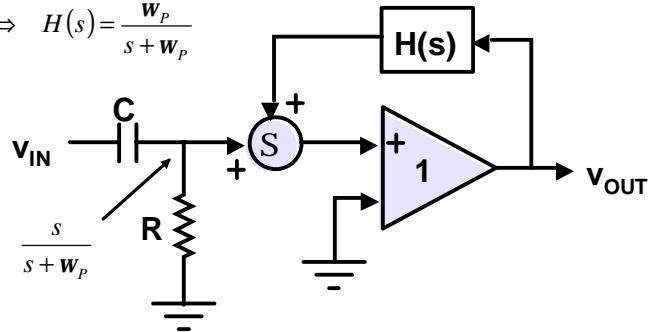
$$\Rightarrow H(s) = \frac{w_p}{s + w_p}$$




Quantized Feedback

 - Quantized feedback uses a low pass filtered version of the decision circuit output to eliminate the high pass function
- dc offset is blocked




Quantized Feedback

 - Though not as simple to visualize, the simplified circuit below does precisely the same thing




Quantized Feedback Output

 

Digital Quantized Feedback

 
- Analog-digital hybrids can also provide baseline wander correction
- The $H(z)$ block maps a logic-level v_{OUT} to channel signal levels
 - 6-7 DAC bits span the full v_{IN} range
- Startup and v_{IN} - v_{OUT} level mismatches must be carefully modeled



Decision Circuits

- Decision circuits generate square wave outputs at the output of the receiver
 - The square wave outputs typically drive a clocked, cross-coupled CMOS latch which produces full logic level swings [4]
- Decision circuits convert all sources of vertical eye degradation into horizontal eye degradation
 - A decision circuit's output transitions between two binary levels at a process-limited (NOT a data rate-limited) speed

Decision Circuit Eye Diagram

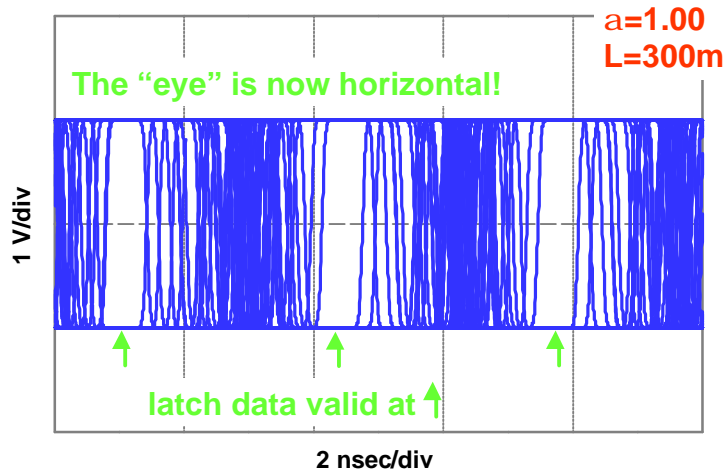

Decision Circuit Eye Diagram

- Obviously the bit error rate depends critically on the position of the green arrows
 - Those are generated by the clock recovery circuit
 - Typically those use an analog or digital PLL
 - We will leave that for 142!

The End

- We've looked at filters, converters, communication circuits ...
- But especially we looked at how to model them
 - To come up with good architectures
 - To invent at the architecture level
 - To evaluate system performance at a high level where changes are manageable
- Good luck and good circuits, and thanks for taking my class!



References

1. Alan Baker, "An Adaptive Cable Equalizer for Serial Digital Video Rates to 400Mb/sec", ISSCC Dig. Tech. Papers, 39, 1996, pp. 174-175.
2. F. D. Waldhauer, "Quantized Feedback in an Experimental 280Mb/s Digital Repeater for Coaxial Transmission", IEEE Trans. on Communications, COM-22, January 1974, pp. 1-5.
3. Dave Pietruszynski, John Steininger, and E. J. Swanson, "A 50Mbit/sec CMOS Monolithic Optical Receiver", IEEE JSSC, SC-23, December 1988.
4. Akira Yukawa, "A CMOS 8-Bit, High-Speed A/D Converter IC", IEEE JSSC, SC-20, June 1985.

