

Pipelined A/D Converter

- Model
- Digital Correction
- Digital Calibration

 A/D DSP EECS 247 Lecture 18: Pipelined ADC



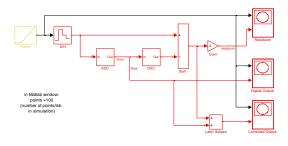





$$V_{res} = G(V_{in} - DV_{ref})$$


See Matlab/Simulink L18_pipe_3_el.mdl


A/D DSP


EECS 247 Lecture 18: Pipelined ADC

 


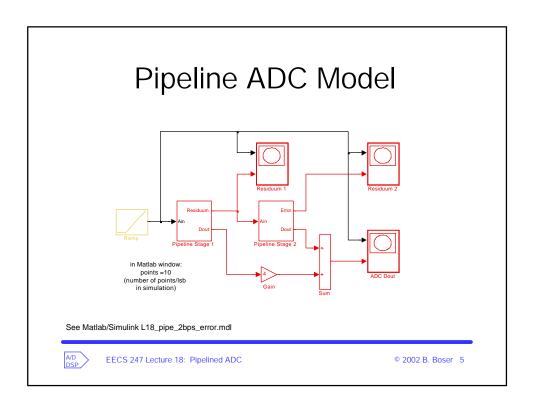


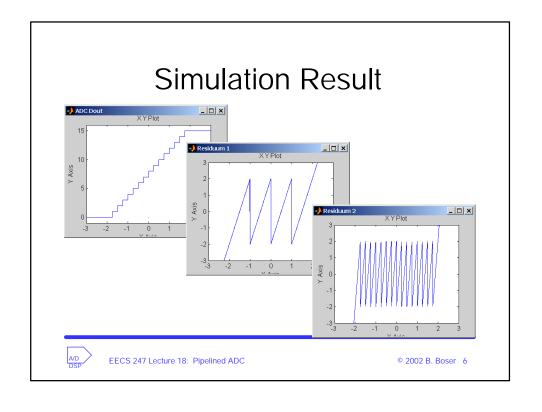


 


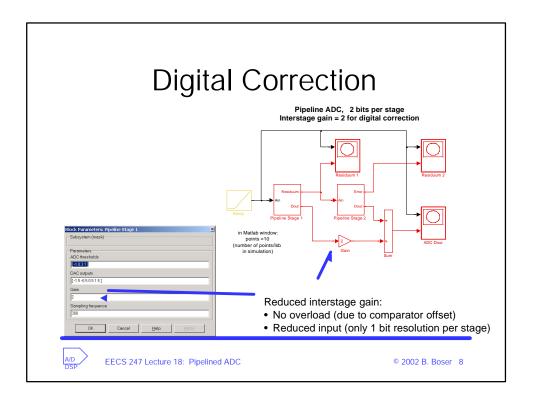

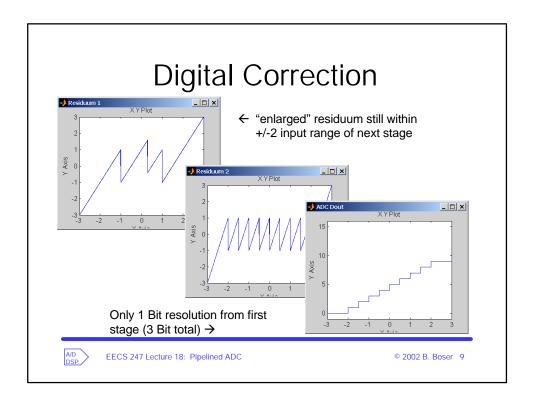

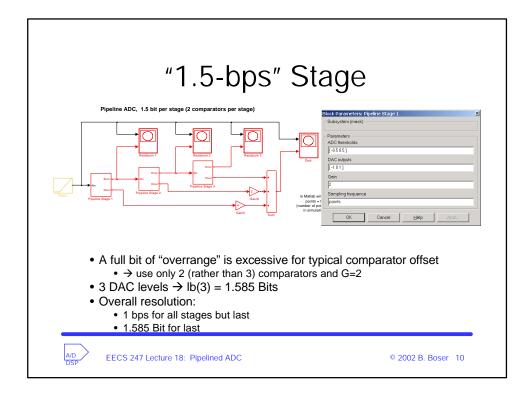

 

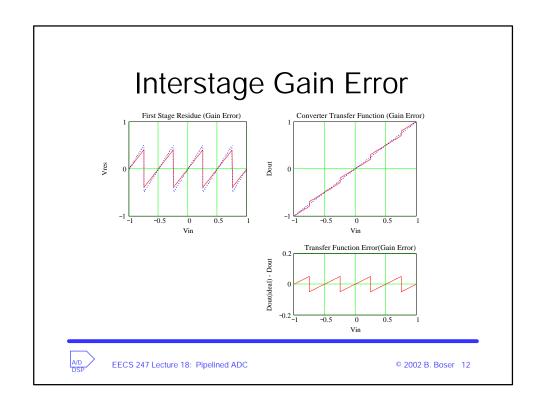

Digital Gain Calibration

· Operation of the pipeline stage:

$$V_{res} = G(V_{in} - DV_{ref})$$

The gain G is off from it's correct value (e.g. 1.8 instead of 2)

· Digital output from the ADC

$$GV_{in} = DGV_{ref} + V_{res}$$

- Gain error (GV_{in} term)
- Nonlinearity at segment boundary (DGV_{ref} term)



EECS 247 Lecture 18: Pipelined ADC


© 2002 B. Boser 13

Digital Gain Calibration

$$GV_{in} = DGV_{ref} + V_{res}$$

- The "digital" gain in the circuit at right is still 2
- The actual amplifier gain in stage 1 is smaller or larger due to component mismatch

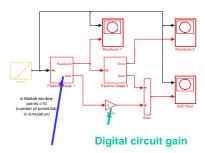 Hence the overall output is incorrect, regardless of the accuracy of stage 2



Analog circuit gain



EECS 247 Lecture 18: Pipelined ADC

Measuring GV_{ref}

- If we knew the value of GV_{ref}, we could use use that in our digital logic, rather than G=2
- How can we measure GV_{ref}?

$$\begin{split} V_{resA} &= V_{res} \big(V_{in} = V_x, D = 0 \big) = GV_x \\ V_{resB} &= V_{res} \big(V_{in} = V_x, D = 1 \big) = GV_x - GV_{ref} \\ V_{resA} - V_{resB} &= GV_{ref} \end{split}$$

- If we proceed from the back of the pipeline, we can use the already calibrated backend to digitize GV_{ref}!
- The measurement is performed once at startup, the values stored in a small RAM (one per stage for 1-bps stage resolution)
- The digital logic uses adders to sum up the different values of GV_{ref} from the table stored in the RAM

A/D DSP EECS 247 Lecture 18: Pipelined ADC


© 2002 B. Boser 15

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 28, NO. 12, DECEMBER 1993

1207

A 15-b 1-Msample/s Digitally Self-Calibrated Pipeline ADC

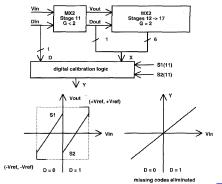Andrew N. Karanicolas, Member, IEEE, Hae-Seung Lee, Senior Member, IEEE, and Kantilal L. Bacrania, Member, IEEE



- 1-Bit per stage
- Only 1 comparator per stage
- G<2 to avoid overload in presence of comparator offset
- Digital gain calibration

A/D DSP

EECS 247 Lecture 18: Pipelined ADC