

# 2<sup>nd</sup> Order Transfer Functions

- Imaginary axis zeroes
- Tow-Thomas Biquad
- Example

## Imaginary Axis Zeros

- Sharpen transition band
- “notch out” interference
- High-pass filter (HPF)
- Band-reject filter


$$H(s) = K \frac{1 + \left(\frac{s}{w_z}\right)^2}{1 + \frac{s}{w_p Q_p} + \left(\frac{s}{w_p}\right)^2}$$

$$|H(jw)|_{w \rightarrow \infty} = K \left(\frac{w_p}{w_z}\right)^2$$


Note: Always represent transfer functions as a product of a gain term, poles, and zeros (pairs if complex). Then all coefficients have a physical meaning, reasonable magnitude, and easily checkable unit.

# Imaginary Axis Zeros

No finite zeros

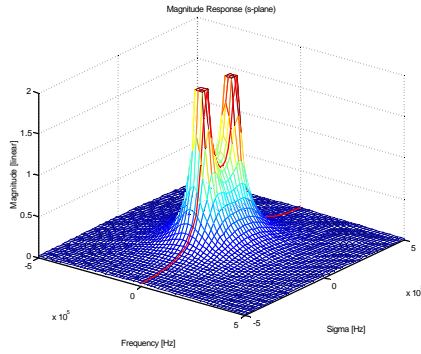

With finite zeros

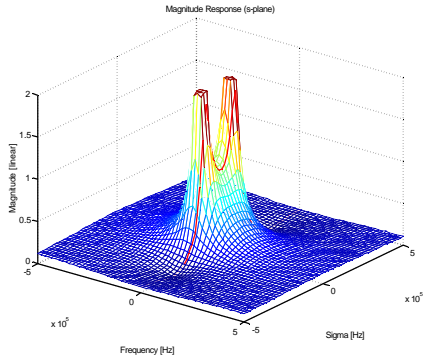



# Imaginary Zeros

$$f_p = 100\text{kHz}$$

$$Q_p = 2$$

$$f_z = 3f_p$$

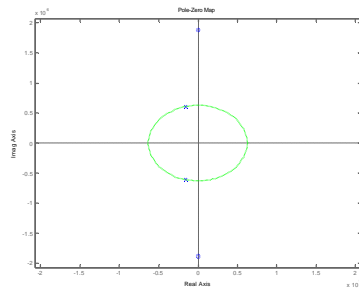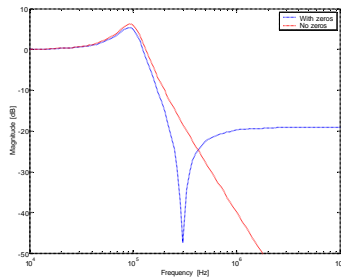- Zeros substantially sharpen transition band
- At the expense of reduced stop-band attenuation at high frequency





# Moving the Zeros


$$f_p = 100\text{kHz}$$

$$Q_p = 2$$

$$f_z = f_p$$

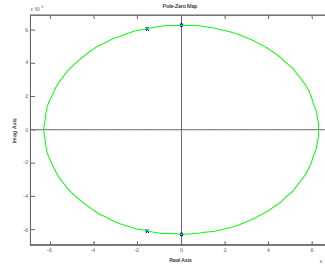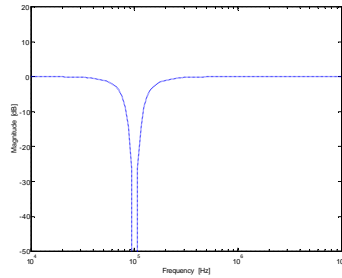

# Tow-Thomas Biquad

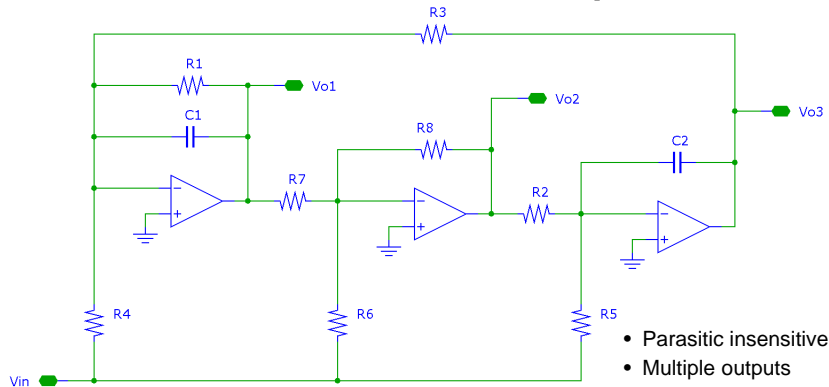

Ref: P. E. Fleischer and J. Tow, "Design Formulas for biquad active filters using three operational amplifiers," Proc. IEEE, vol. 61, pp. 662-3, May 1973.

# Frequency Response

$$\frac{V_{o1}}{V_{in}} = -k_2 \frac{(b_2 a_1 - b_1)s + (b_2 a_0 - b_0)}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o2}}{V_{in}} = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o3}}{V_{in}} = -\frac{1}{k_1 \sqrt{a_0}} \frac{(b_0 - b_2 a_0)s + (a_1 b_0 - a_0 b_1)}{s^2 + a_1 s + a_0}$$

- $V_{o2}$  implements a general biquad section with arbitrary poles and zeros
- $V_{o1}$  and  $V_{o3}$  realize the same poles but are limited to at most one finite zero

# Component Values

$$b_0 = \frac{R_8}{R_3 R_5 R_7 C_1 C_2}$$

$$b_1 = \frac{1}{R_1 C_1} \left( \frac{R_8}{R_6} - \frac{R_1 R_8}{R_4 R_7} \right)$$

$$b_2 = \frac{R_8}{R_6}$$

$$a_0 = \frac{R_8}{R_2 R_3 R_7 C_1 C_2}$$

$$a_1 = \frac{1}{R_1 C_1}$$

$$k_1 = \sqrt{\frac{R_2 R_8 C_2}{R_3 R_7 C_1}}$$

$$k_2 = \frac{R_7}{R_8}$$

given  $a_i, b_i, k_i, C_1, C_2$  and  $R_8$

$$R_1 = \frac{1}{a_1 C_1}$$

$$R_2 = \frac{k_1}{\sqrt{a_0} C_2}$$

$$R_3 = \frac{1}{k_1 k_2} \frac{1}{\sqrt{a_0} C_1}$$

$$R_4 = \frac{1}{k_2} \frac{1}{a_1 b_2 - b_1} \frac{1}{C_1}$$

$$R_5 = \frac{k_1 \sqrt{a_0}}{b_0 C_2}$$

$$R_6 = \frac{R_8}{b_2}$$

$$R_7 = k_2 R_8$$

it follows that


$$w_p = \sqrt{\frac{R_8}{R_2 R_3 R_7 C_1 C_2}}$$

$$Q_p = w_p R_1 C_1$$

# Filter Design Example

- Application: testing of ultra-linear ADC
- Problem: sinusoidal source has higher distortion than the ADC!
- Solution
  - Filter source with bandpass before converting
  - Check resulting source with spectral analyzer  
Twist: the analyzer is not sufficiently linear either  
→ notch out sinusoid and look just at harmonics
- Implementation
  - Bandpass & Notch at 1kHz
  - Use  $V_{o2}$  for bandpass (only possibility),  $V_{o1}$  for notch

# Filter Design Example

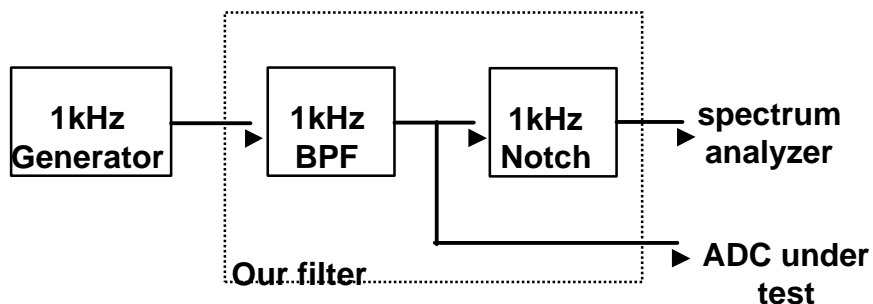

**Principle: IC test circuits are useless if you can't verify their performance!**

# Filter Coefficients

$$\frac{V_{o1}}{V_{in}} = -k_2 \frac{(b_2 a_1 - b_1)s + (b_2 a_0 - b_0)}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o2}}{V_{in}} = \frac{b_2 s^2 + b_1 s + b_0}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o3}}{V_{in}} = -\frac{1}{k_1 \sqrt{a_0}} \frac{(b_0 - b_2 a_0)s + (a_1 b_0 - a_0 b_1)}{s^2 + a_1 s + a_0}$$

Design Notch:

$$b_0 = a_0 = \omega_p^2 = (2\pi \times 1\text{kHz})^2$$

$$b_1 = 0$$

$$b_2 = 1$$

Get Bandpass for "free":

$$b_2 a_1 - b_1 = a_1$$

$$b_2 a_0 - b_0 = 0 \quad (\text{just as we want in a bandpass})$$

Choose reasonable signal levels:

$$k_1 = 1.05 \quad (\text{to keep unused } V_{o3} \text{ slightly below other outputs})$$

$$k_2 = 1$$



# Final Filter

Choose:

C1=C2=112nF (large to minimize noise)

R8=1kΩ

f<sub>p</sub>=1kHz, Q<sub>p</sub>=30 (check sensitivity!)

$$\frac{V_{o1}}{V_{in}} = -\frac{a_1 s}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o2}}{V_{in}} = \frac{s^2 + a_0}{s^2 + a_1 s + a_0}$$

$$\frac{V_{o3}}{V_{in}} = -\frac{1}{1.05} \frac{a_1 \sqrt{a_0}}{s^2 + a_1 s + a_0}$$

Solve equations ...

R1=42.631kΩ

R2=1.4921kΩ

R3=1.3534kΩ

R4=42.631kΩ

R5=1.4921kΩ

R6=R7=R8

Let's order the parts ...



# Capacitors

- COG capacitors
  - Vishay Vitramon, COG Dielectric Capacitor datasheet, 2000.  
<http://www.vishay.com/document/45002/45002.pdf>
  - Negligible voltage coefficient (for linearity)
  - Excellent tempco (30ppm/°C)
  - 2% initial accuracy is easy to get
- No high-value capacitors are trimmable
- Resistors will be trimmed to compensate for capacitor variations



# Resistors


- Trimmed resistors combine fixed metal film resistors and precision trim potentiometers in series
  - 1%-accurate, 5ppm/°C, lab grade metal film resistors provide ~90% of the nominal resistance  
  
Ref: Caddock Electronics, Type TN Lab Grade Low TC Precision Film Resistor datasheet, 1999.
  - 50ppm/°C trim pots provide between 0% and ~20% of the nominal resistance  
  
Ref: Vishay Foil Resistors, Model 1268 Precision Trimming Potentiometers datasheet
  - Use two fixed resistors in series with the trimpot to minimize trimpot value and optimize overall tempco
- R6-R8 are 0.1%-accurate, 5ppm/°C metal film



# Opamps

- For opamps, we'll use the Burr-Brown OPA627
  - Ref: Texas Instruments / Burr-Brown, OPA627 and OPA604 datasheets, 1989.
  - The finest audio opamp in the world, and, at \$15/each, priced accordingly!
  - But money is no object when designing IC test fixtures (only a few are ever built)
  - Adequate speed for this application

## Bandpass/Bandstop Responses

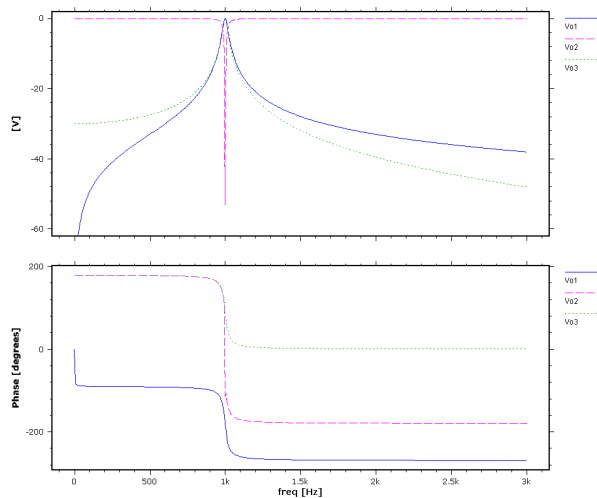




## Filter Design Example (cont.)

- Note that the bandpass output  $H_1$  provides  $>30\text{dB}$  attenuation to all harmonics present in the 1kHz generator output
- Opamp outputs have  $0.0\pm 0.5\text{dB}$  peak gain
  - This maximizes each opamp's output swing for best dynamic range
- Let's magnify the frequency axis for the two responses of interest...


## Bandpass/Bandstop Responses

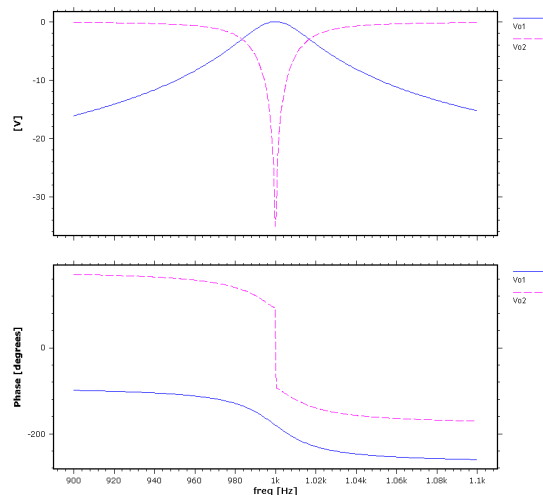

# Filter Design Example

- Temperature changes won't change these responses too much
  - Lab temperatures are stable to  $25 \pm 3^\circ\text{C}$
  - Our lab-grade RC products move  $<100\text{ppm}/^\circ\text{C}$
- Initial component values are another story
  - What if  $C_1=114\text{nF}$  and  $C_2=113\text{nF}$ ?
  - That's within their  $\pm 2\%$  accuracy specifications
  - What's  $S_{C_1}^{W_P}$  ?

## Bandpass/Bandstop Responses

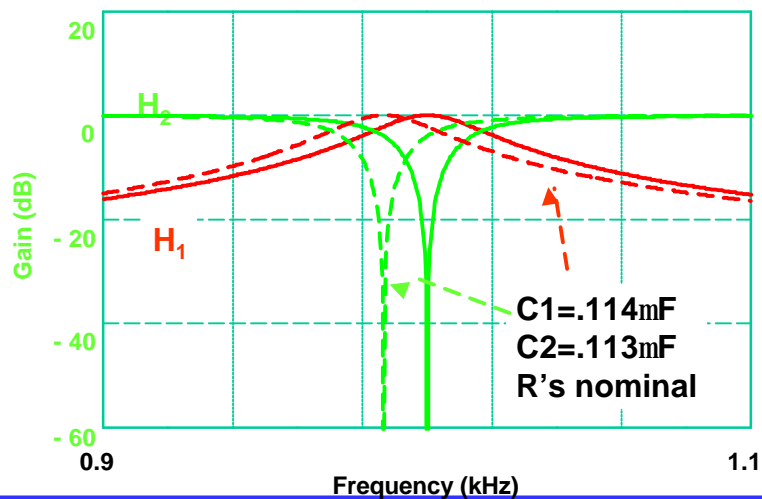

# Filter Design Example

- Obviously, we've got to tune the filter back to its original specification
- How is that tuning done?
  - Do you tell your technician to twiddle pots randomly until it works?
  - Or do you document a robust tuning procedure?

# RC Filter Tuning Strategy

- Famous biquads like the Tow-Thomas come complete with their own tuning strategies
  - The circuit topologies allow 1 trim operation to adjust 1 design parameter (such as  $f_p$ ,  $f_z$ ,  $Q_p$ ,  $Q_z$ , gain) without changing the others
- Rationale for a biquad's tuning strategy becomes apparent when studying design equations such as the Tow-Thomas equations on slide 6

## Tow-Thomas Tuning Strategy

- R3 will be set to a fixed value to keep the unused OPAMP3 output below 0dB
- Tuning involves the following steps performed in the specified sequence:
  - Adjust R2 to center the bandpass at 1kHz
  - Adjust R5 to center the notch at 1kHz
  - Adjust R1 to set the bandpass Q to 30
  - Adjust R4 to deepen the notch

## Tow-Thomas Tuning Strategy

- The design equations also provide the range of adjustment required for a given resistor
  - Remember that an excessively large adjustment range translates into excessively large tempco
- R1 tuning range (from slide 7):

$$a_1 \circ \frac{1}{R_1 C_1} \text{ D } \frac{1}{a_1 C_{1\text{MAX}}} < R_1 < \frac{1}{a_1 C_{1\text{MIN}}}$$


known

set by capacitor tolerances

# Tow-Thomas Tuning Strategy

- An even simpler way to determine resistor ranges is to:
  - Set all capacitors to their high tolerance limit (nominal+2% in this case)
  - Calculate R's for these capacitances (these will be the minimum resistance values)
  - Set capacitors to their low tolerance limit
  - Calculate maximum R's


# Tow-Thomas Biquad

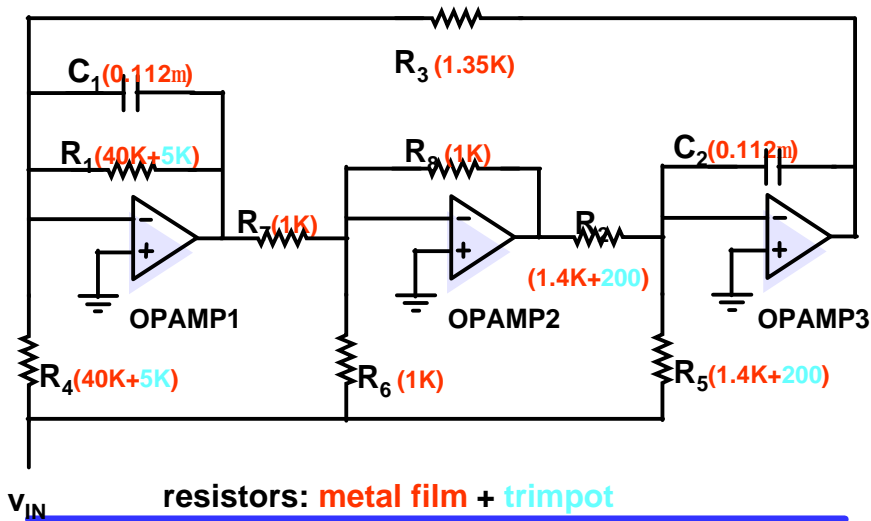


# Tow-Thomas Tuning Strategy

- If you've left your filter unattended for a while, assume that its trim potentiometers are completely misadjusted
- Adjust all trimpots to  $0\Omega$  and start over
  - Let's return to our  $C1=114\text{nF}$ ,  $C2=113\text{nF}$  example

# Bandpass/Bandstop Responses

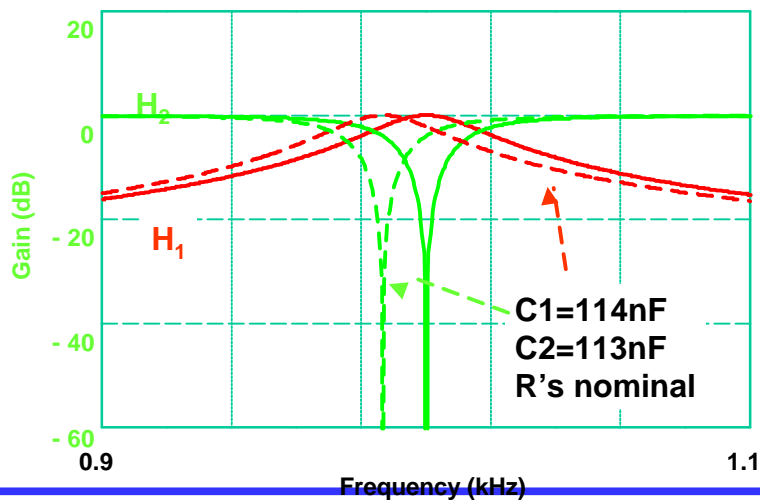

## Bandpass/Bandstop Responses

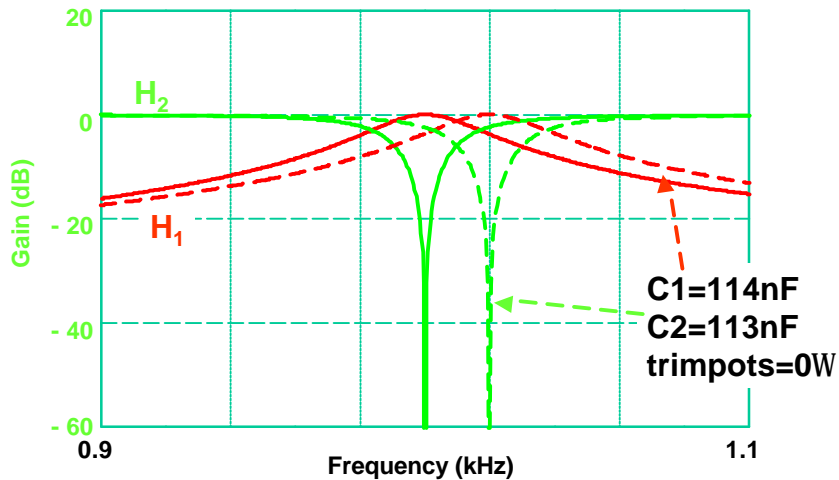

## Tow-Thomas Tuning Strategy


- For most R's and C's in this biquad  $f_p \sim \frac{1}{\sqrt{x}}$

- Hence,

$$S_x^{f_p} = -\frac{1}{2}$$

- This means a +2% change in  $R_2$  will cause a -1% change in  $f_p$
- Note that  $f_z$  sensitivities are also  $-1/2$ 
  - A 4% increase in  $R_5$  will shift our notch (currently at 1.02kHz) back to the right place

## Bandpass/Bandstop Responses

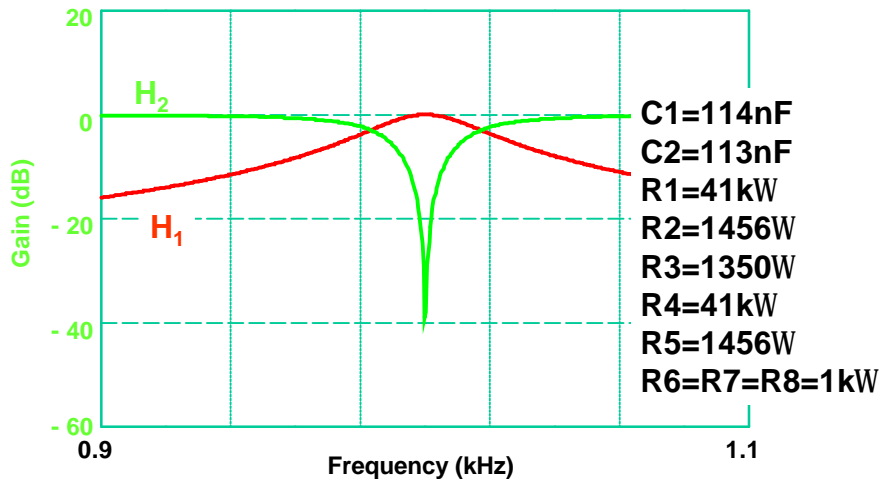

## Summary

- General 2<sup>nd</sup> order transfer function
  - Imaginary axis zeros
- General purpose biquad
  - Large selection in literature
  - Tow-Thomas biquad:
    - 3 opamps
    - Parasitic insensitive
    - Multiple outputs
    - Tuning strategy