Complete Electrical-Port Equiv. Circuit

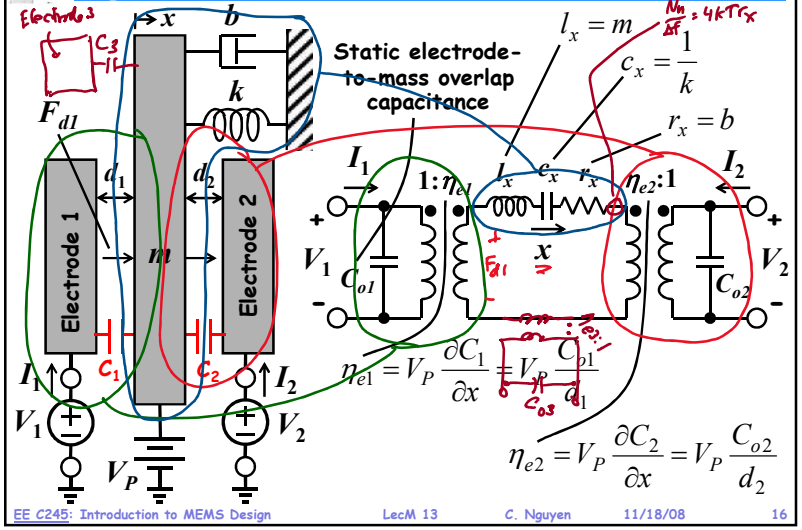

16

Condensed Equiv. Circuit (Symmetrical)

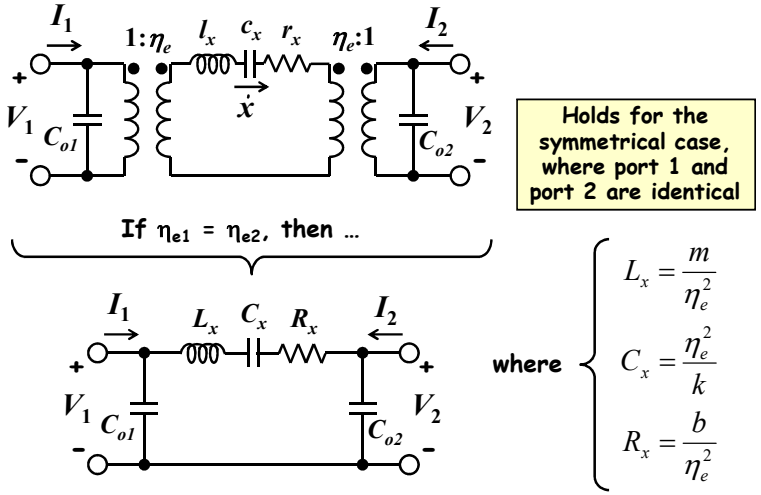

21

Phasings of Signals

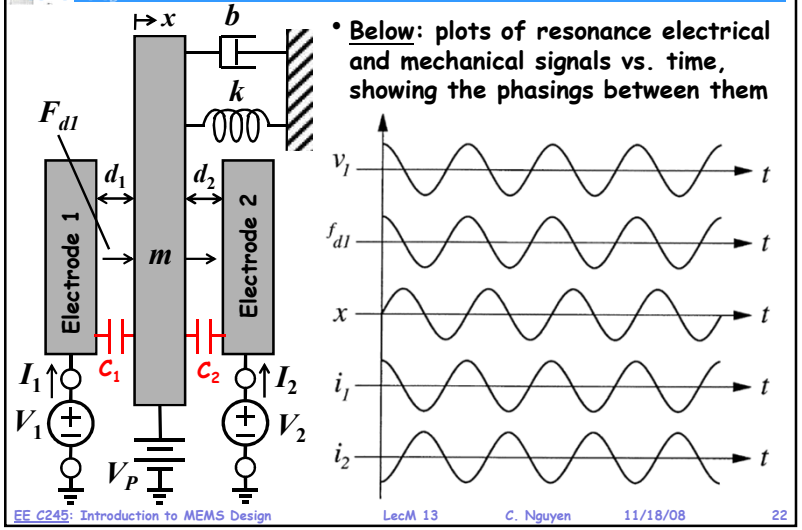

22

Copyright © 2020 Regents of the University of California